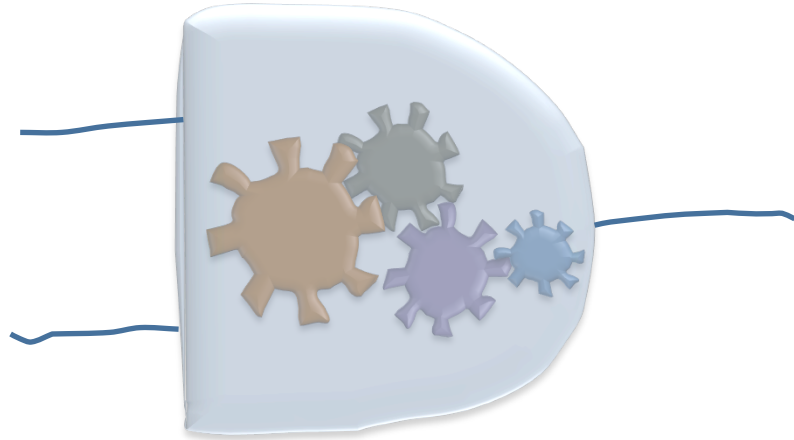


6.002x

CIRCUITS AND ELECTRONICS


Inside the Digital Gate




Reading: Chapter 6 of A&L

Review

The Digital Abstraction

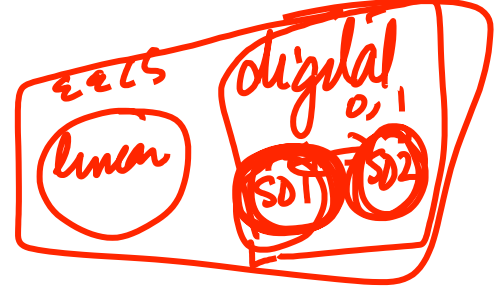

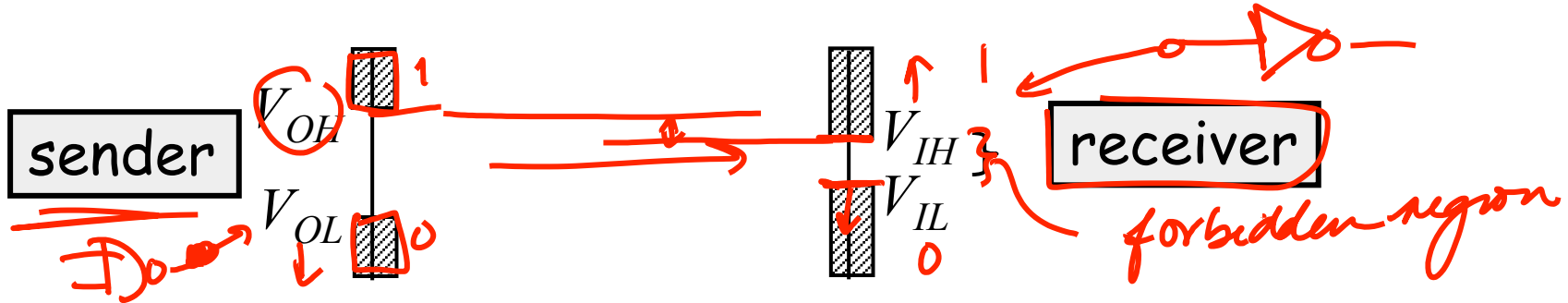- Discretize value: $0, 1$
- Static discipline -- digital devices meet voltage thresholds




Specifies how gates must be designed

Review

Combinational gate abstraction

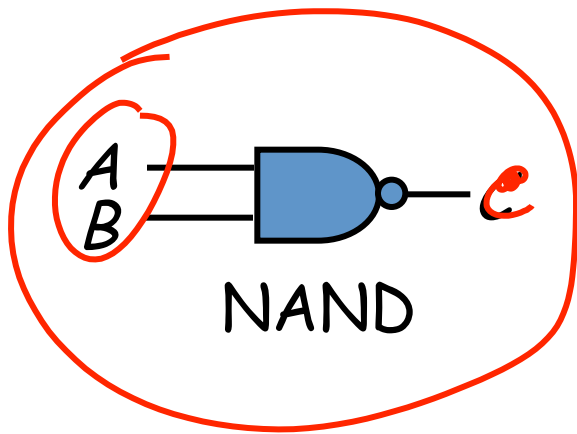- outputs function of input alone
- satisfies static discipline




A	B	C
0	0	1
0	1	1
1	0	1
1	1	0


Truth tables

Review

A digital circuit

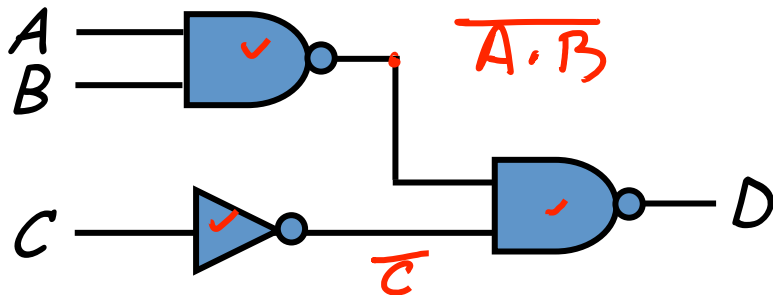

3 gates here

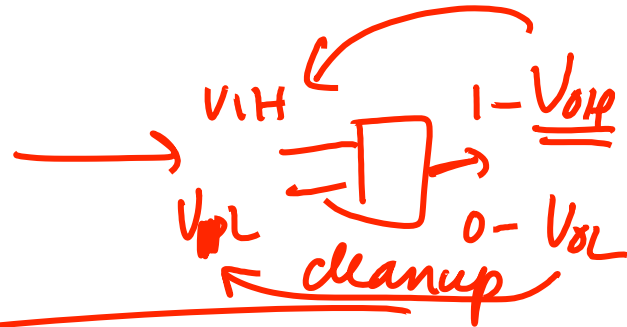


$$((A \cdot B) \cdot C)$$

- A Nehalem class microprocessor from Intel has approx 1 billion gates
- The RAW multicore chip (<http://groups.csail.mit.edu/cag/raw/>) built by students at CSAIL, MIT, had about 3 million gates
- The 64-core Tile processor from Tilera has approx a half billion gates

Review


A digital circuit

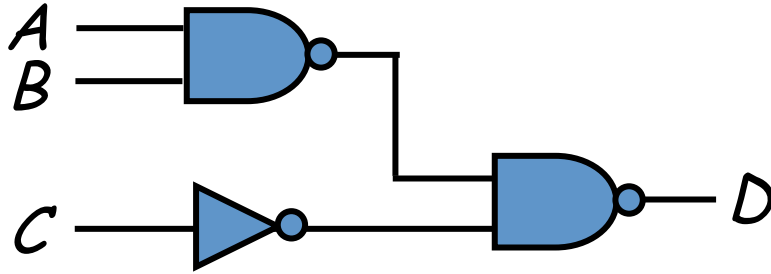

<http://localhost:8000/static/book/p027.jpg>

How to build a digital gate


Analogy

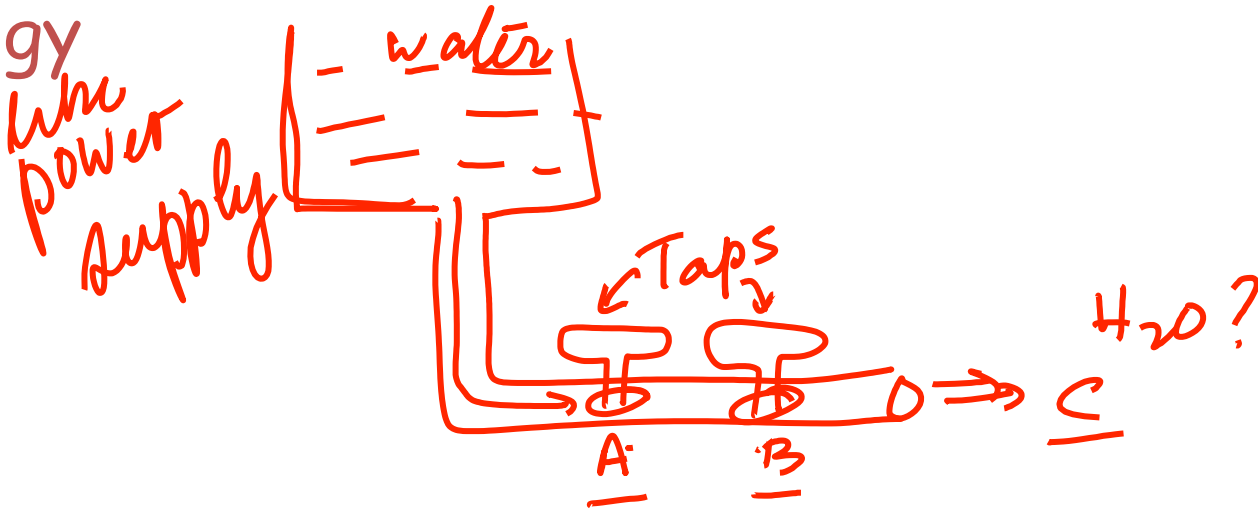


If $A = \text{ON}$ AND $B = \text{ON}$
THEN C has H_2O
else C has no H_2O

Use this
insight to
build an
AND gate.

How to build a digital gate

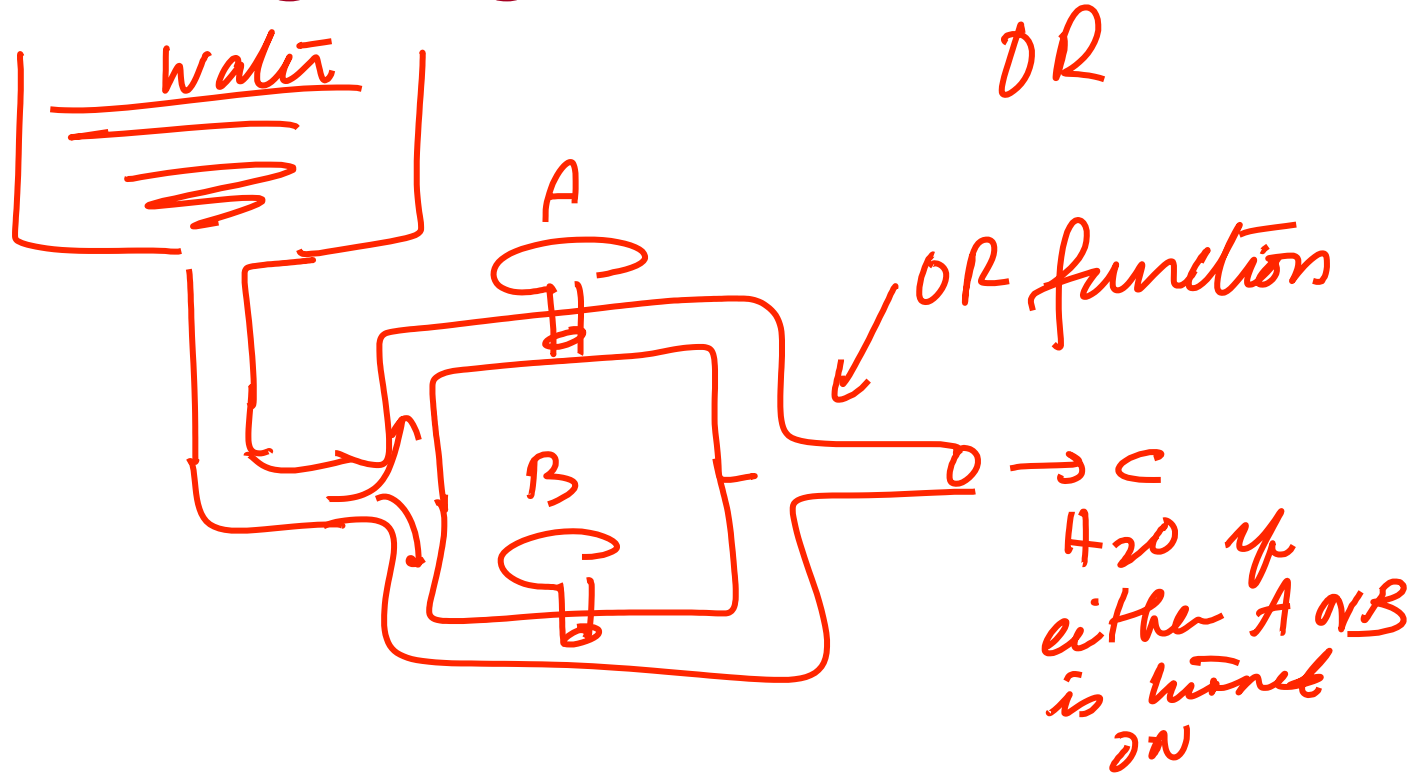

Electrical Analogy

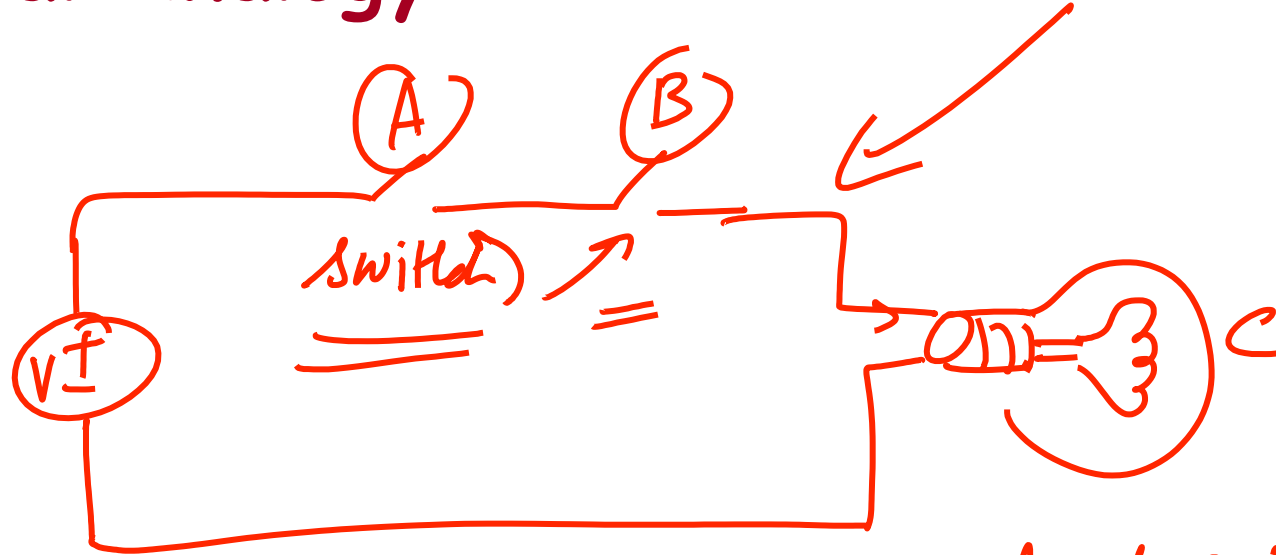


If A AND B are ON, bulb C is ON
else bulb C is off

Key: we need a "switch" device

New Switch Element

Consider abstract
"switch" device

Equivalent ckt

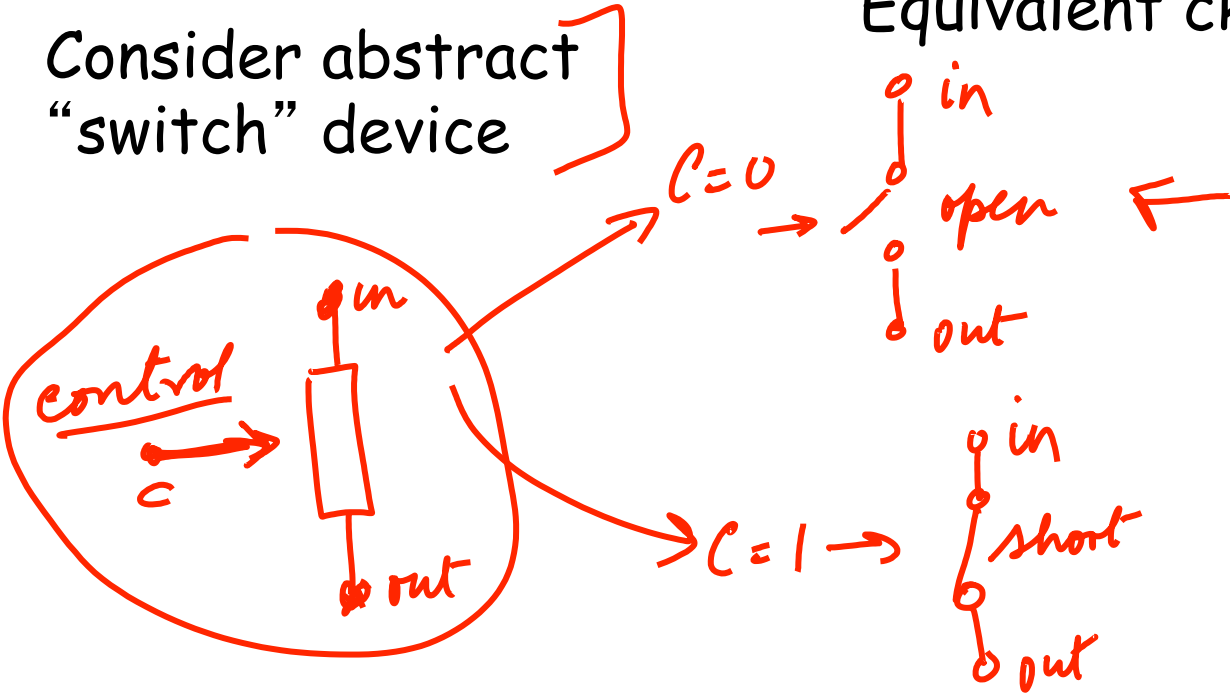

For
mechanical
switch,
control
mechanical
pressure


3-Terminal device

if $C = 0$: short circuit between in and out


else: open circuit between in and out

$\Rightarrow C=0$


Now, consider this circuit

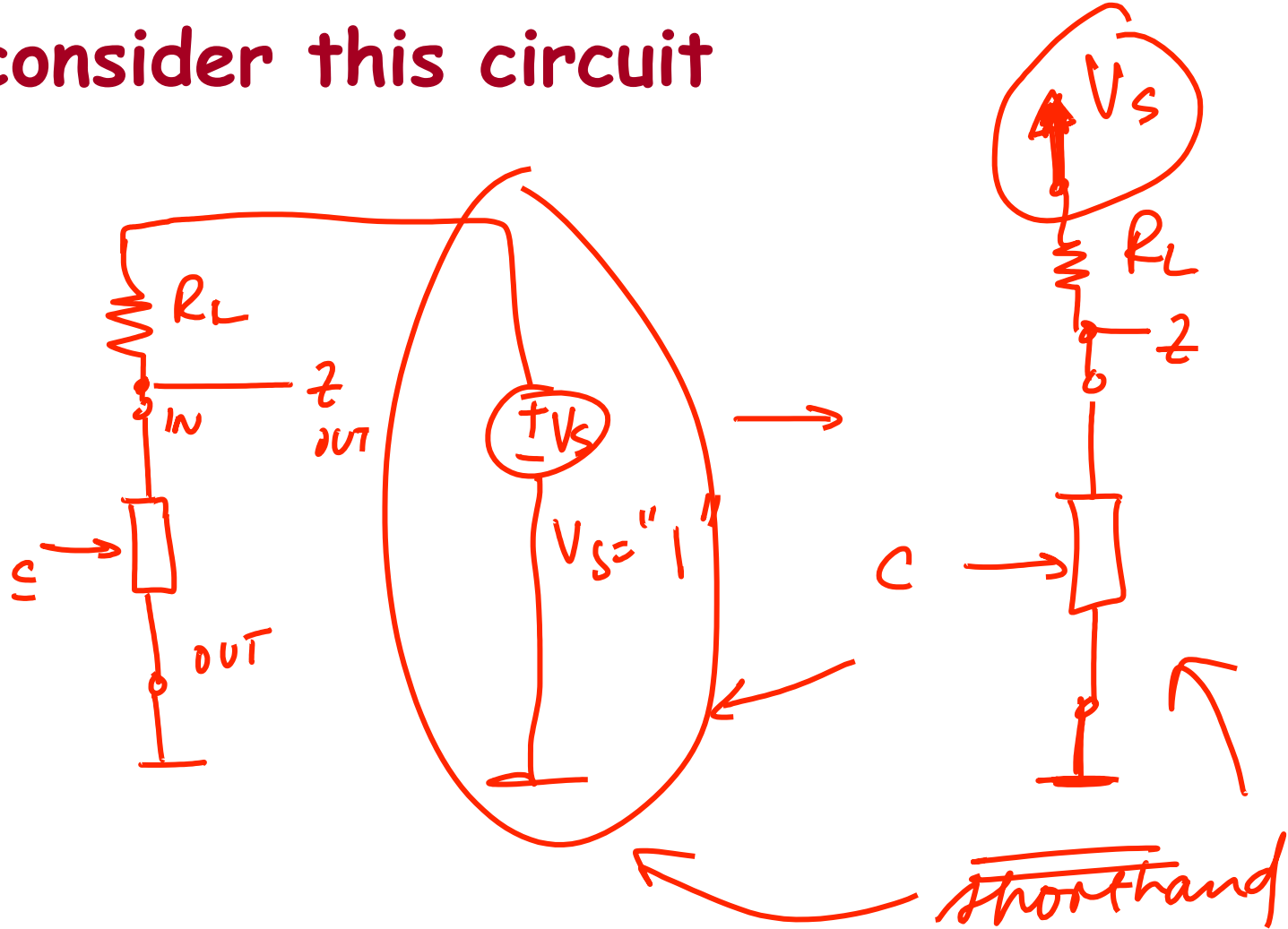



Behavior of this circuit

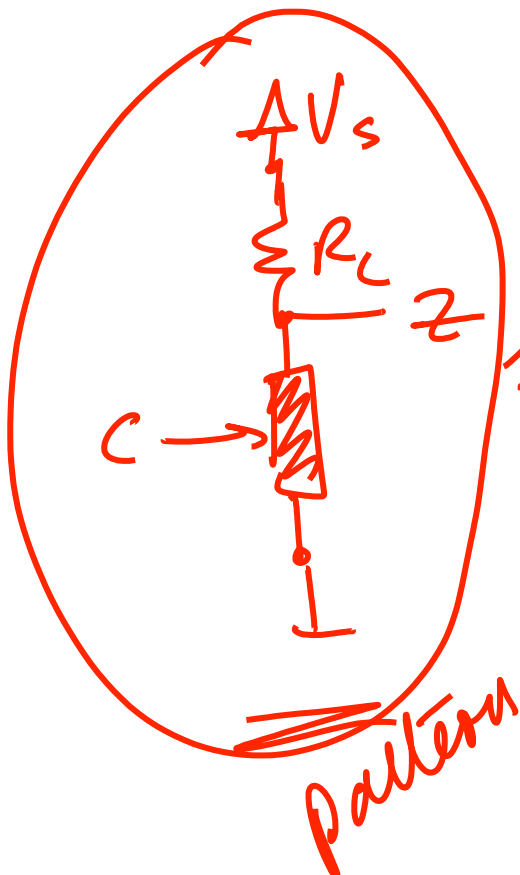

$C = 0 \rightarrow$

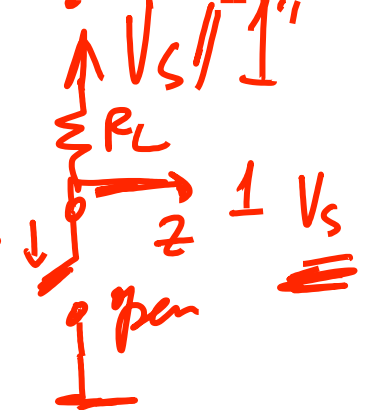


$C = 1 \rightarrow$

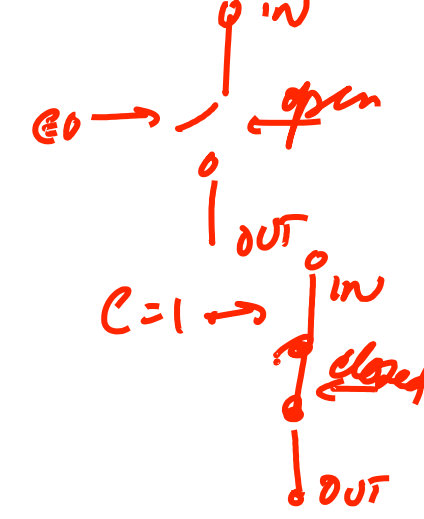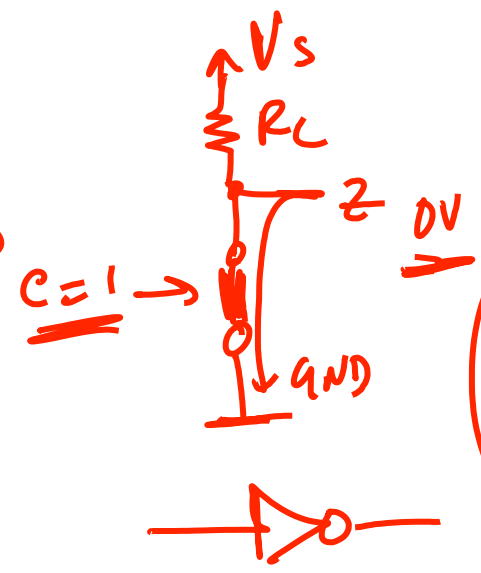

eqn.


C	z
0	1
1	0

What about?

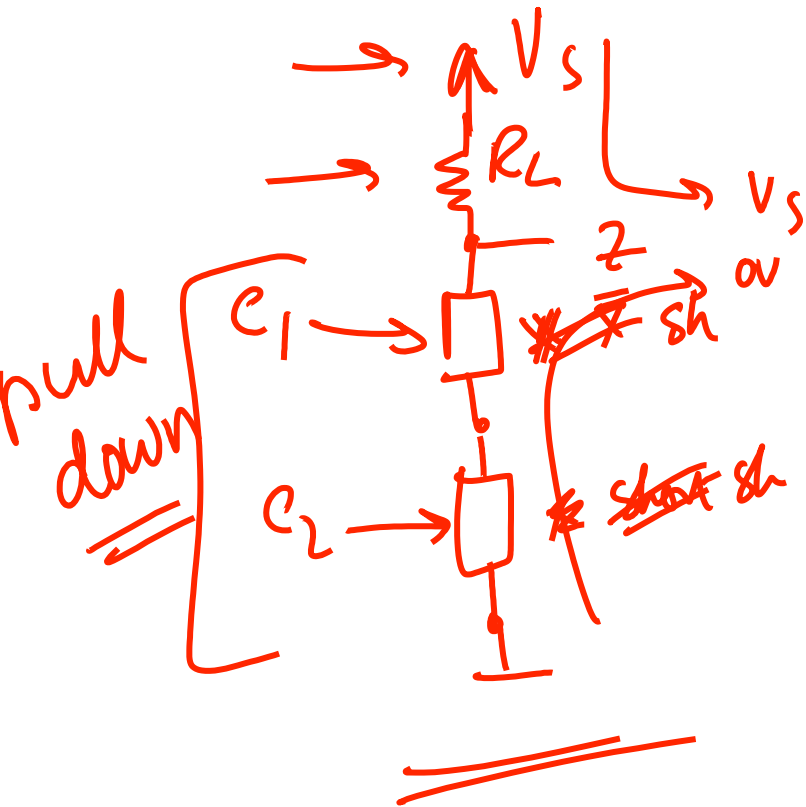


C_1	C_2	z
0	0	1
0	1	1
1	0	1
1	1	0

Truth table for

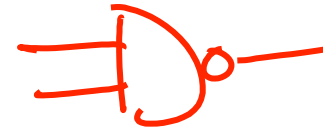


What about?

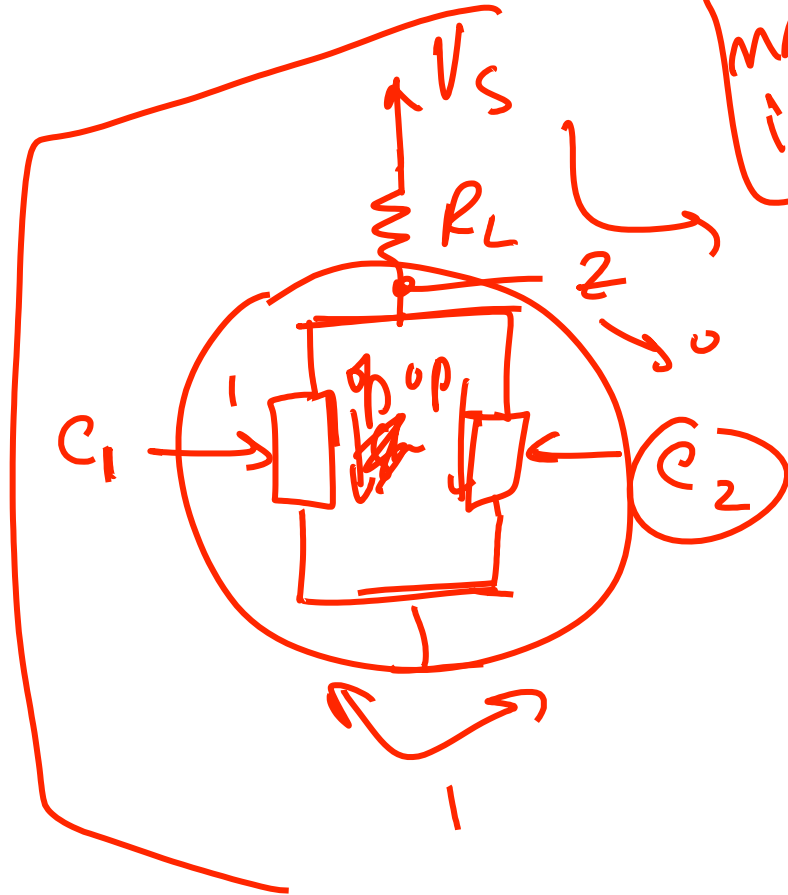


natural inversion

C_1	C_2	Z
0	0	1
0	1	0
1	0	0
1	1	0

Truth Table for ?

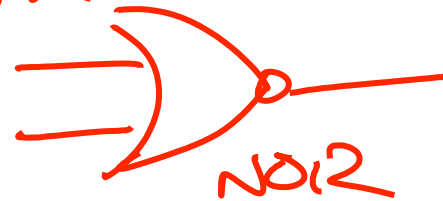

We can also build compound gates

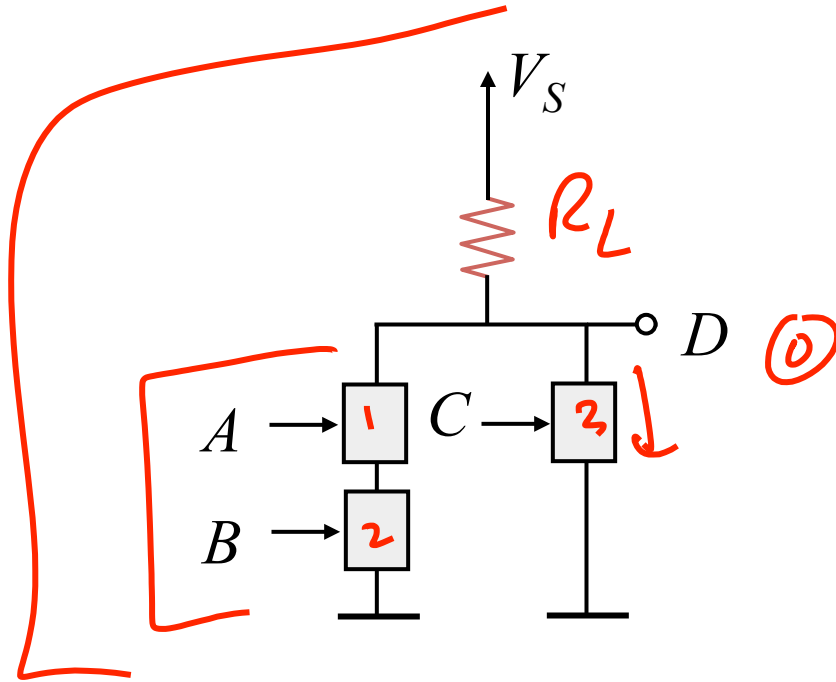

$$D = (A \cdot B) + C$$

magical abstract switch!

Now let's get back to reality... we need a physical switch

The MOSFET Device

~~Do not~~ → ~~Do not~~

Metal-Oxide Semiconductor
Field-Effect Transistor


3 terminal lumped element
behaves like a switch

G: control terminal


D, S: behave in a symmetric
manner (for our needs)

6-002x

Chap 6.7

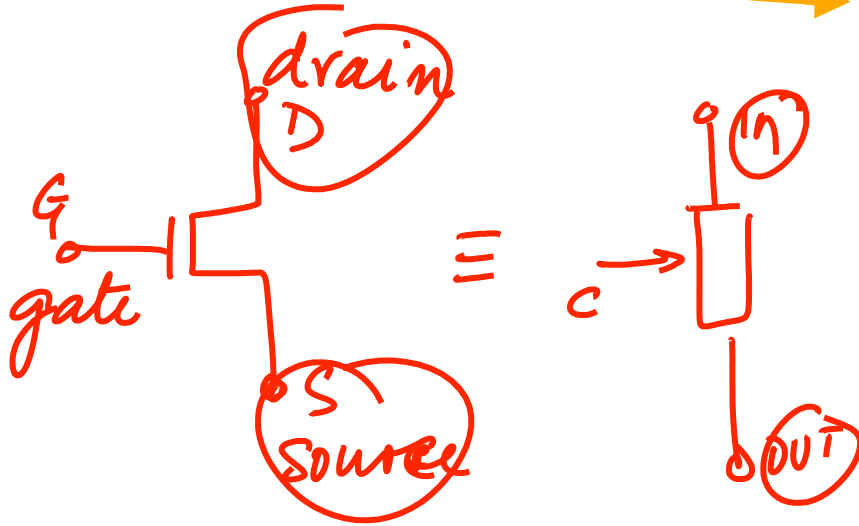

The MOSFET Device

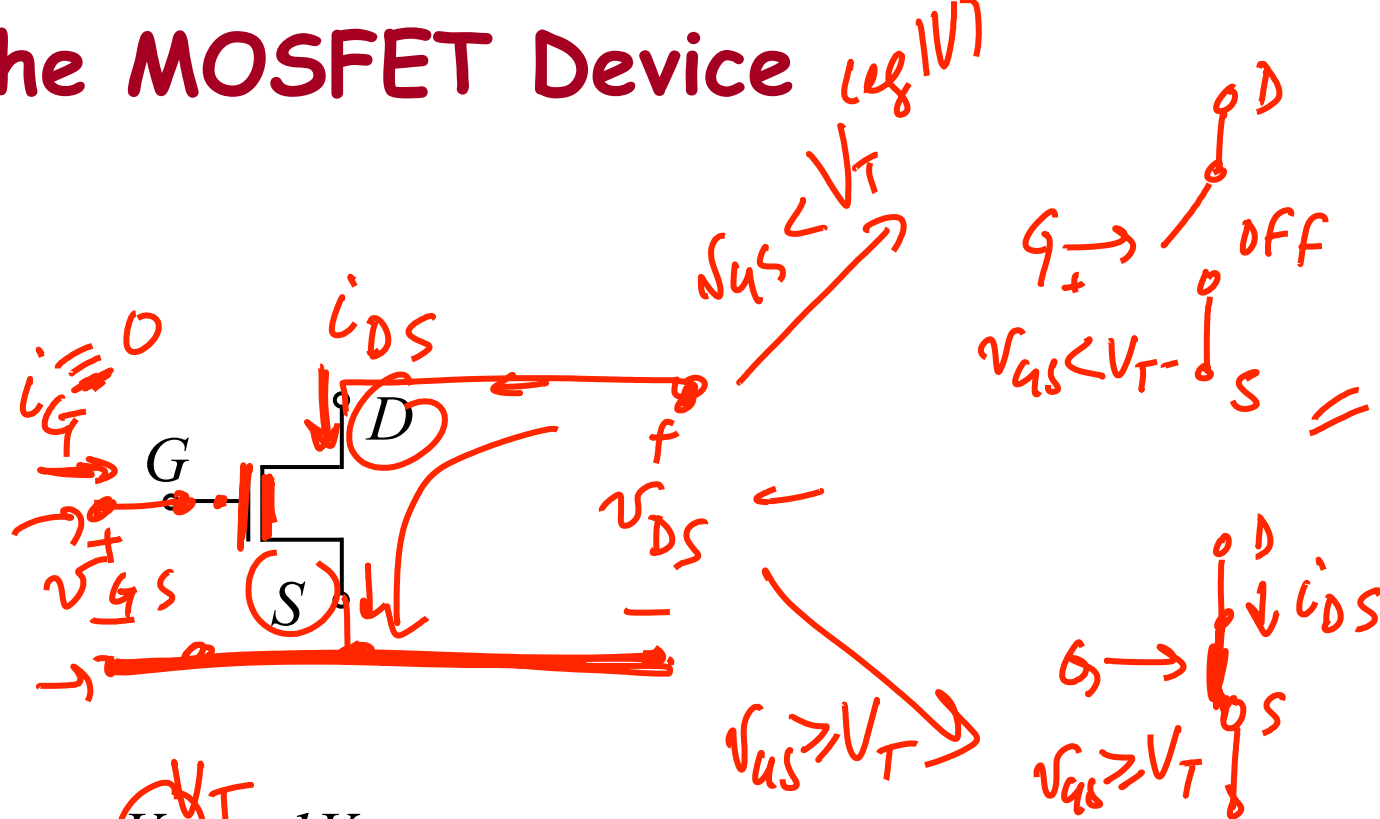



Understand its operation by viewing it as a two-port element

Check ~~text~~ the textbook for its internal structure Sec 6.7

~~MOS~~ but actually more complex!

“Switch” model (S model) of the MOSFET

Check the MOS device on a scope

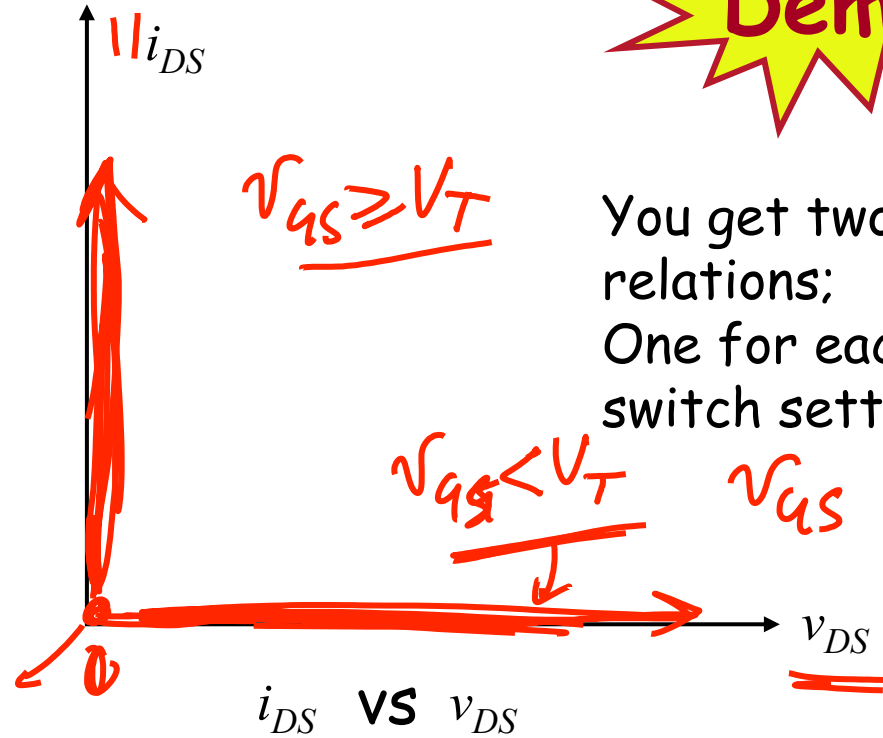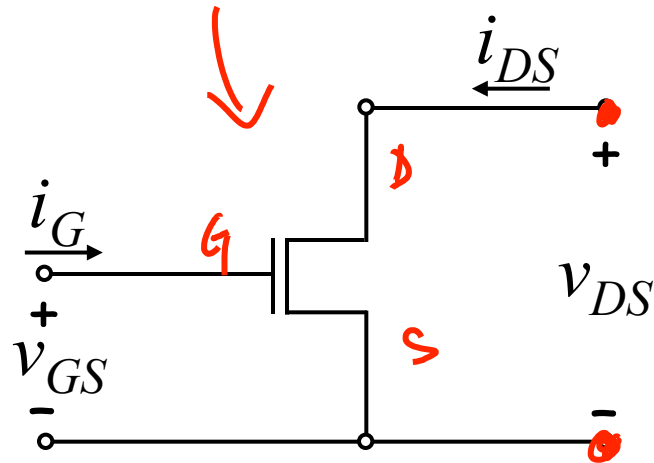


Demo

You get two v-i relations;
One for each switch setting

(As we will see soon, ~~open~~ note that the actual MOSFET behavior is quite a bit more complex. The above switch characterization is a gross simplification. If you cannot wait, check out Section 7.3 of the textbook for the actual MOSFET characteristics)


A MOSFET Inverter

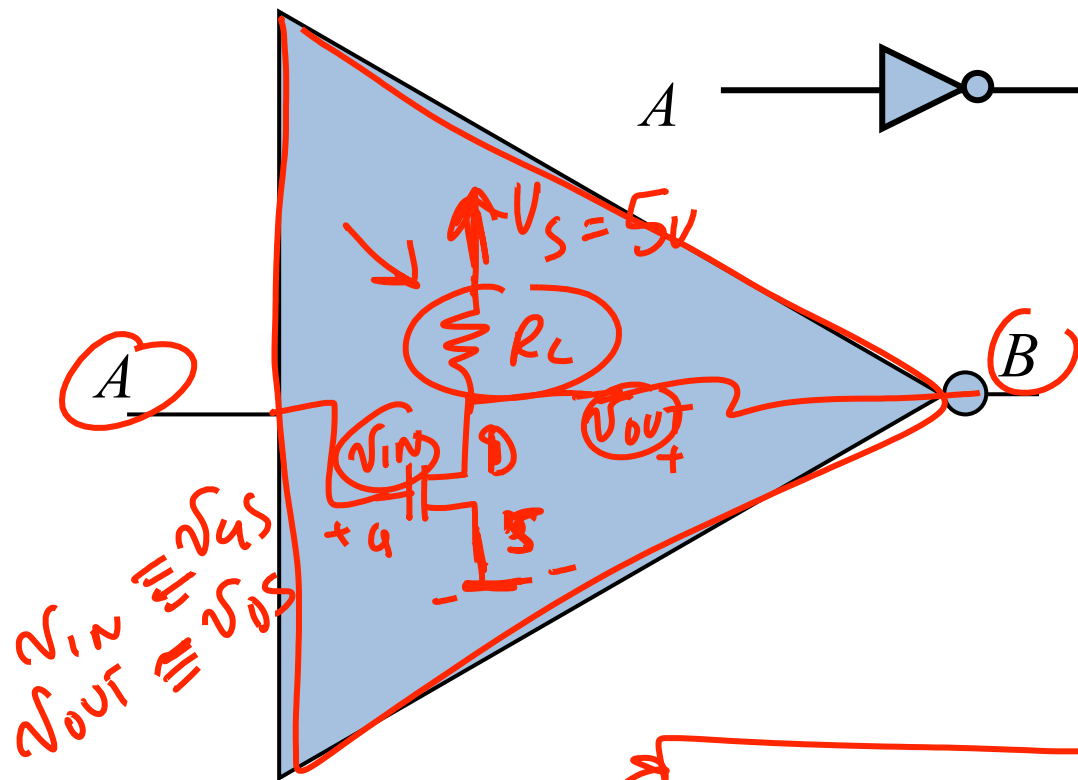




Note the power of abstraction:

The abstract inverter gate representation hides internal details such as power supply connections, R_L , GND , etc. When we build digital circuits, the \uparrow and \perp are common across all gates!

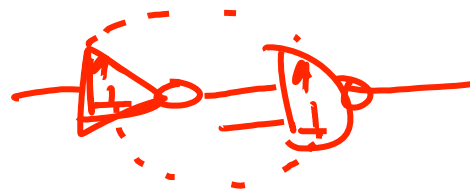A, B : Logic value $0, 1$
 V_{IN} : Voltage value



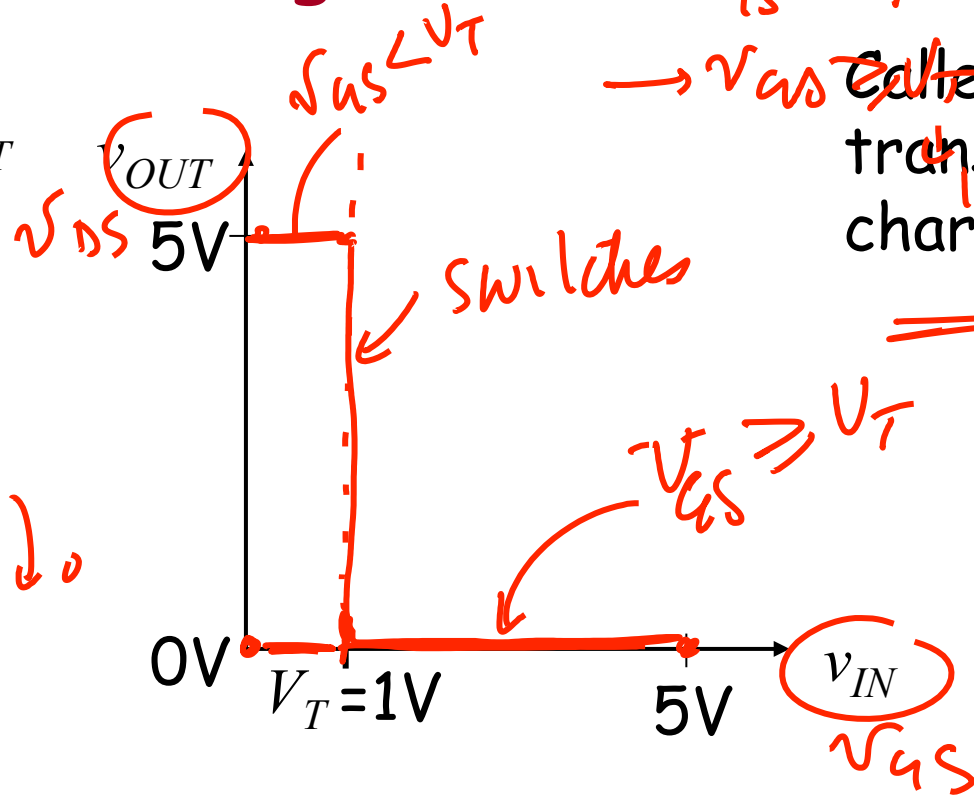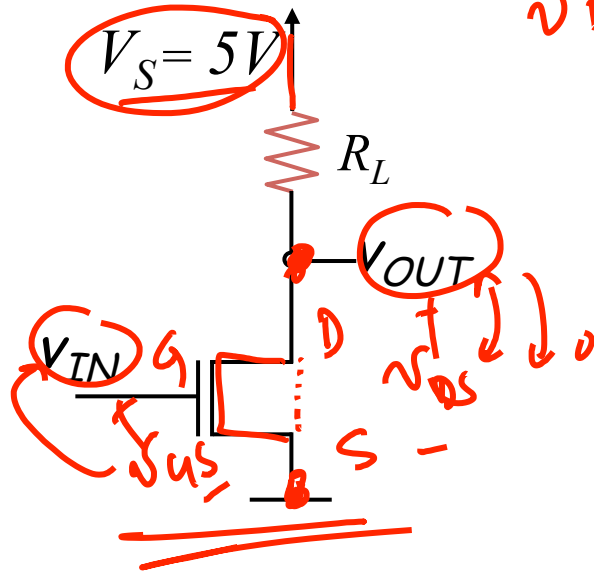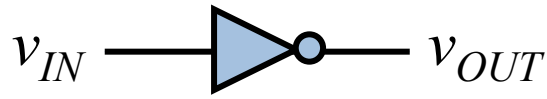We can plot the relationship between the input and output voltages




$\rightarrow v_{GS} < V_T$ open D-S

$\rightarrow v_{GS} \geq V_T$ called short-circuit


transfer characteristic

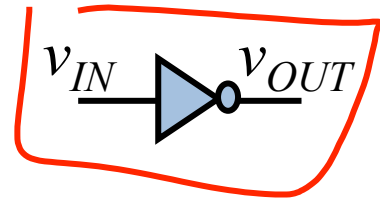Question: The T1000 model laptop needs gates that satisfy a static discipline with voltage thresholds given below. Does our inverter qualify?




$$V_{OL} = 0.5V \quad V_{IL} = 0.9V$$



$$V_{OH} = 4.5V \quad V_{IH} = 4.1V$$

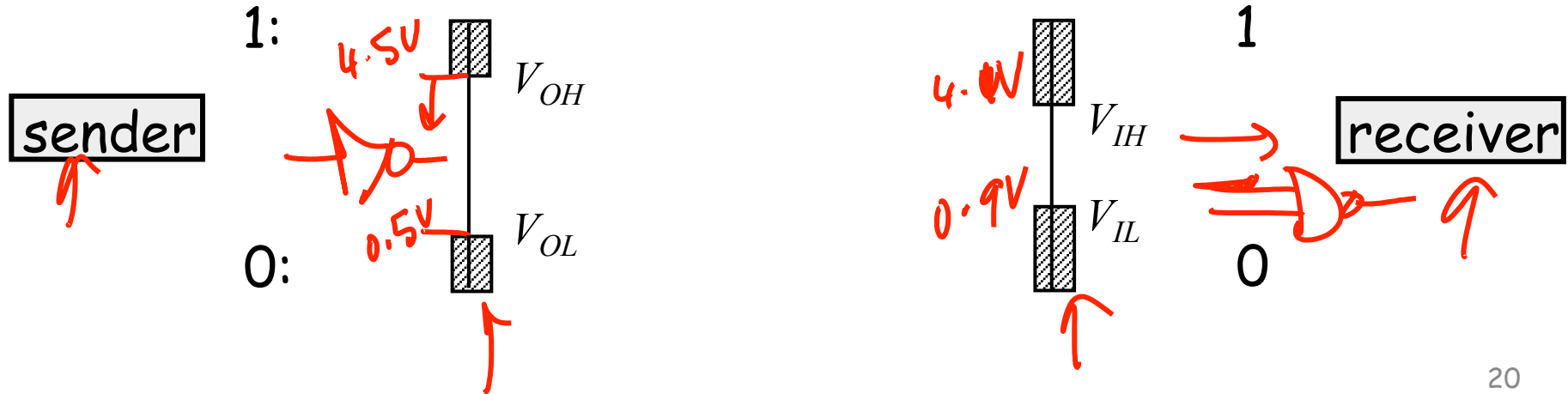


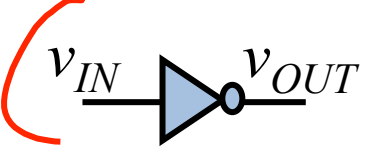
Does our inverter satisfy the voltage thresholds for this static discipline?



$V_{OL} = 0.5V$	$V_{IL} = 0.9V$
$V_{OH} = 4.5V$	$V_{IH} = 4.1V$

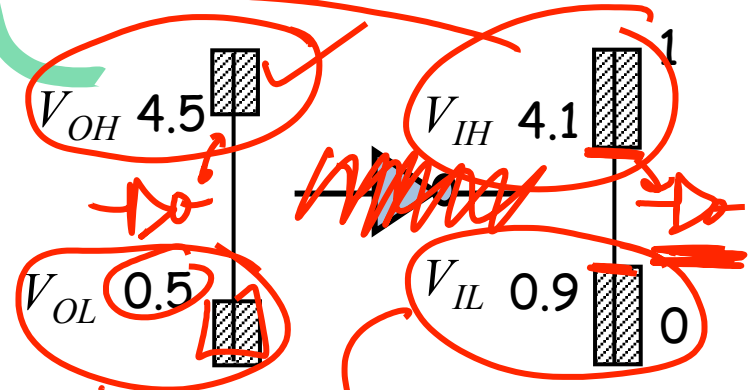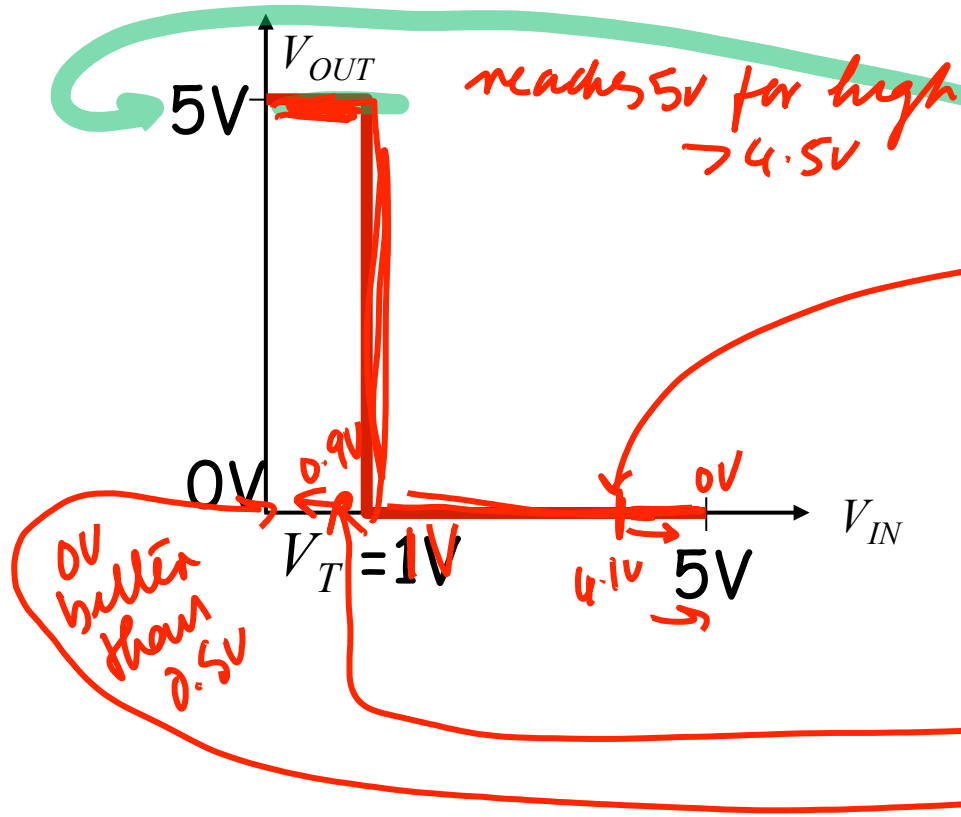

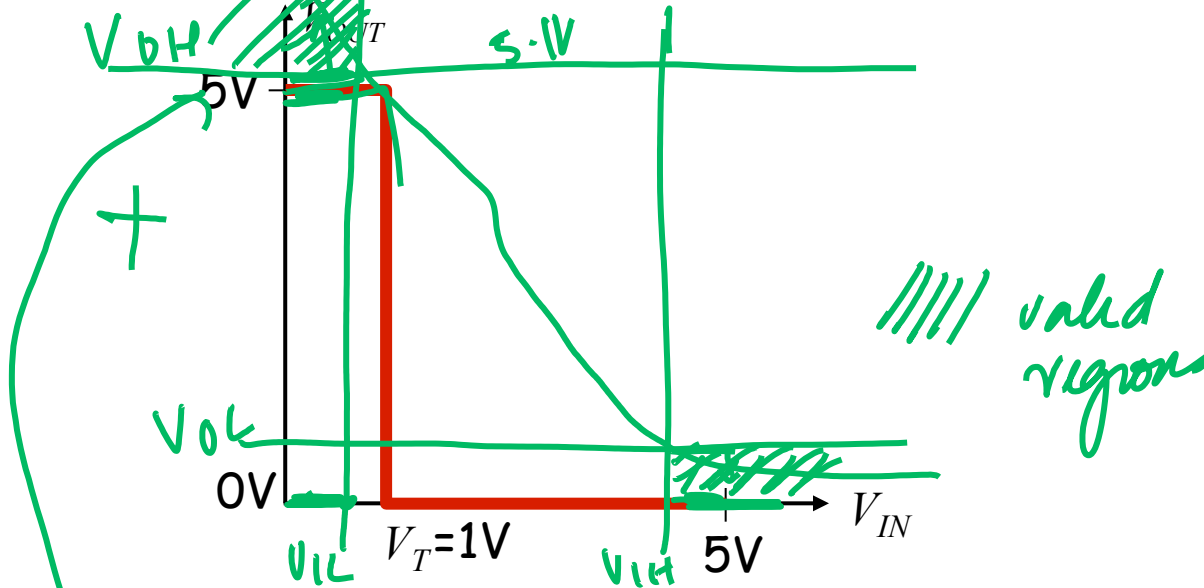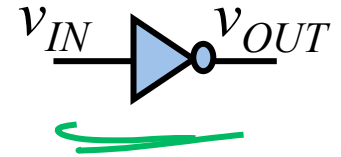Does our inverter satisfy the static discipline for these different thresholds?



$V_{OL} = 0.2V$	$V_{IL} = 0.5V$
$V_{OH} = 5.1V$	$V_{IH} = 4.5V$

NO



$$V_{OL} = 0.2V$$

$$V_{IL} = 0.5V$$

$$V_{OH} = 5.1V$$

$$V_{IH} = 4.5V$$

How about these thresholds?

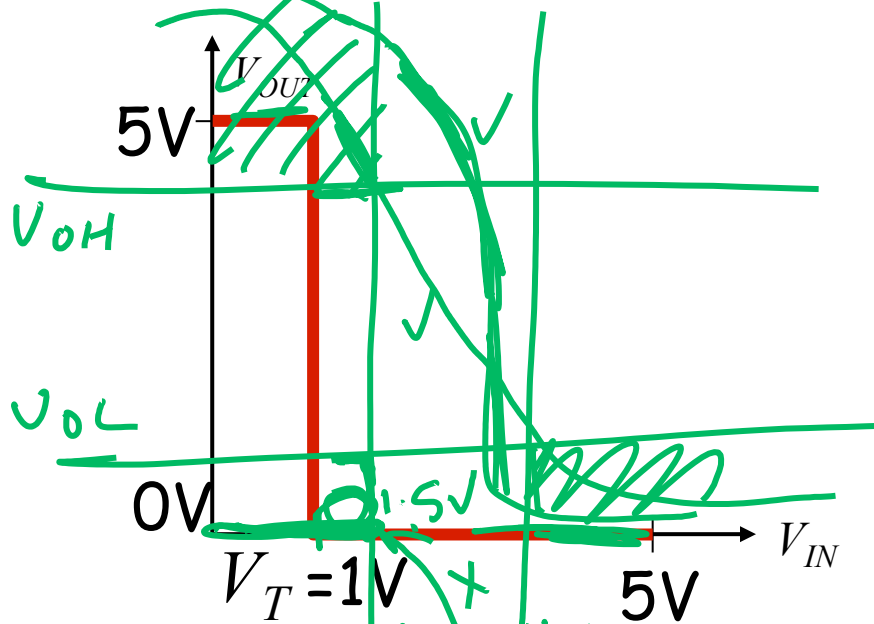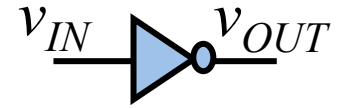

$$V_{OL} = 0.5V \quad V_{IL} = 1.5V$$

$$V_{OH} = 4.5V \quad V_{IH} = 3.5V$$

$$V_{12} \quad \text{---} \quad V_{14}$$

NO!

$$V_{OL} = 0.5V$$




$$V_{II} = 1.5V$$

$$V_{OH} = 4.5V$$

$$V_{IH} = 3.5V$$





Switch Resistor (SR) Model of MOSFET

...a more accurate MOSFET model

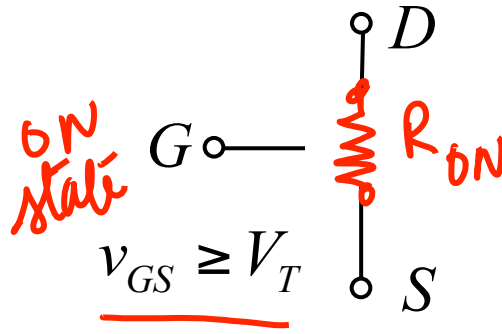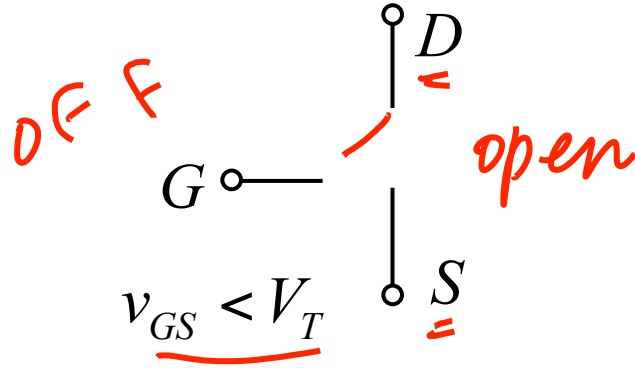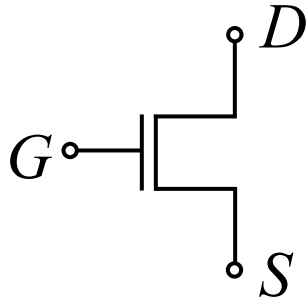


e.g. $R_{ON} = 5k\Omega$

SR Model of MOSFET

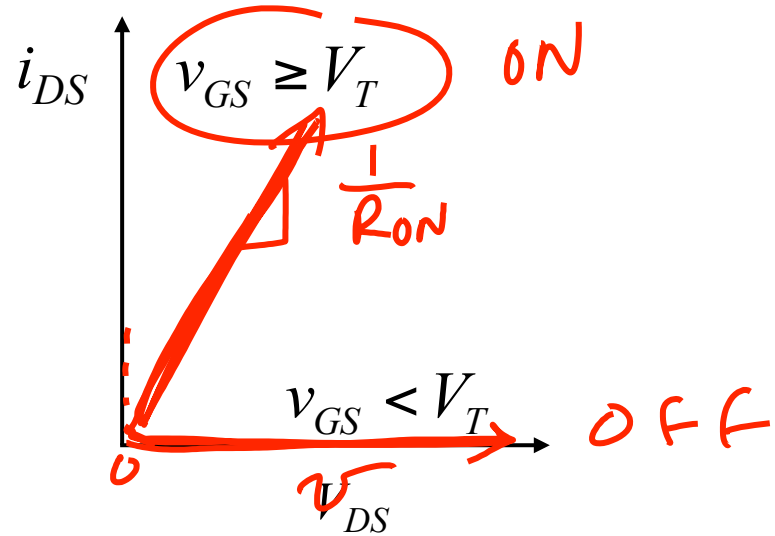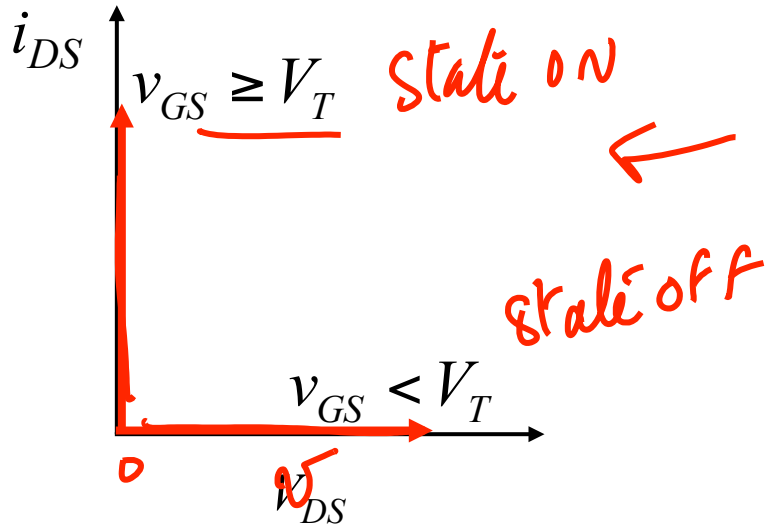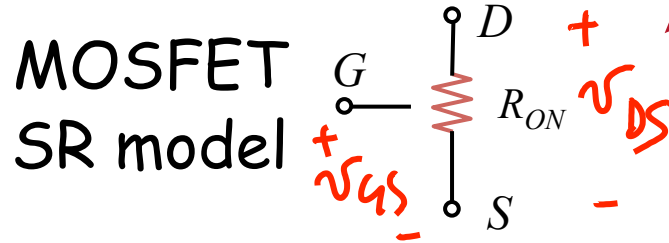
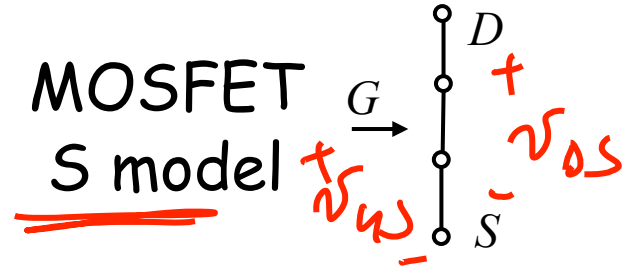


Using the SR model

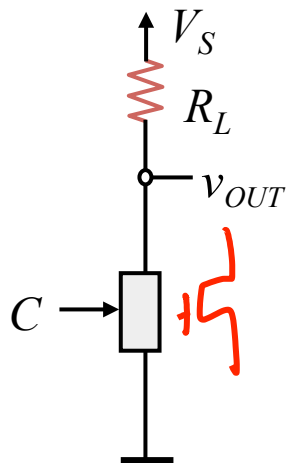

$C = 0$
OUT

$C = 1$

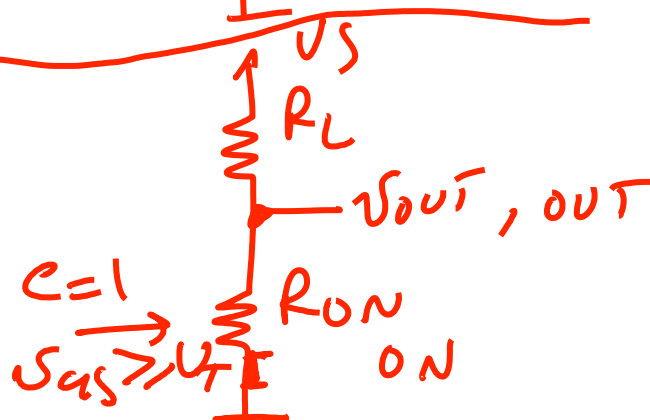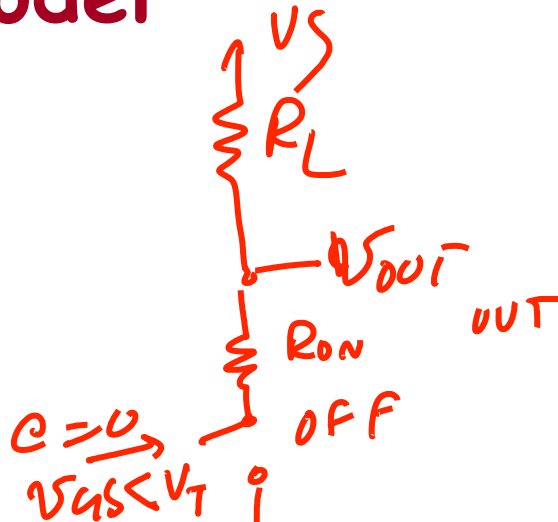





C	OUT
0	1
1	0

Choose R_L, R_{ON}, V_S



$$V_{OUT} = \frac{V_S R_{ON}}{R_L + R_{ON}} \approx V_{OL}$$

$R_{ON} \ll R_L$

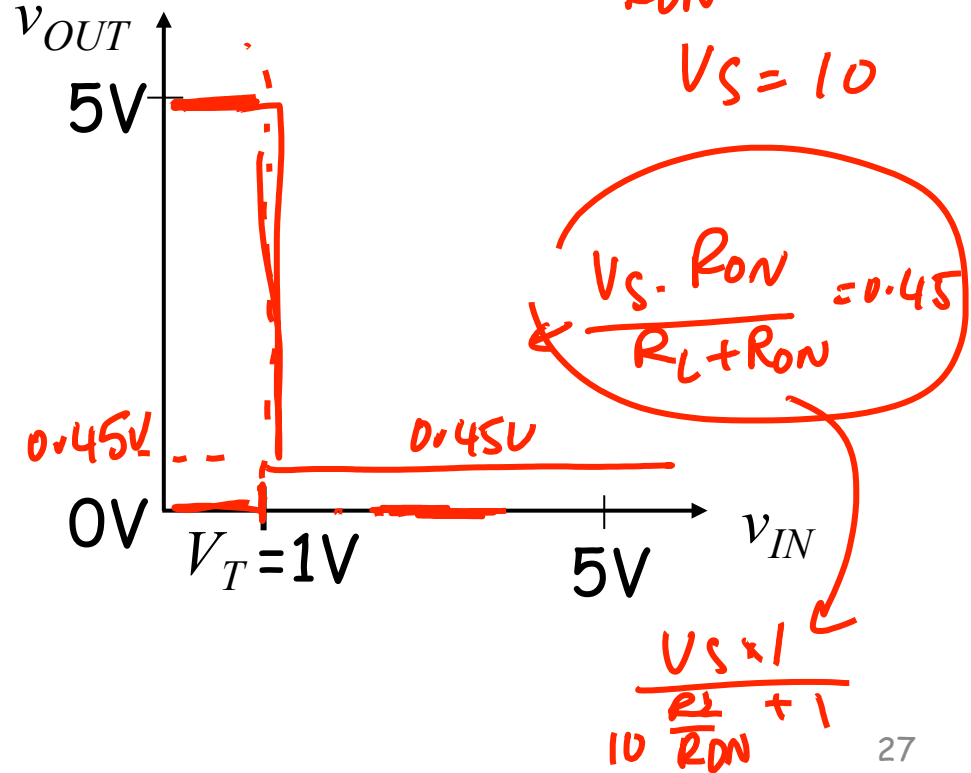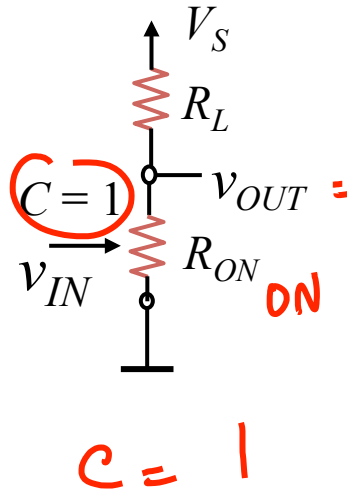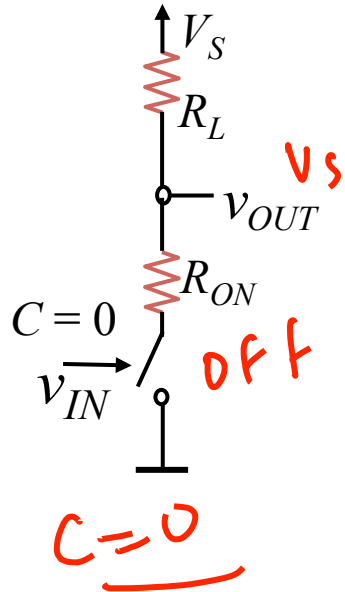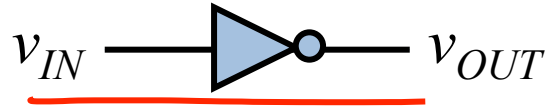
Transfer Function for Inverter using the SR MOSFET Model



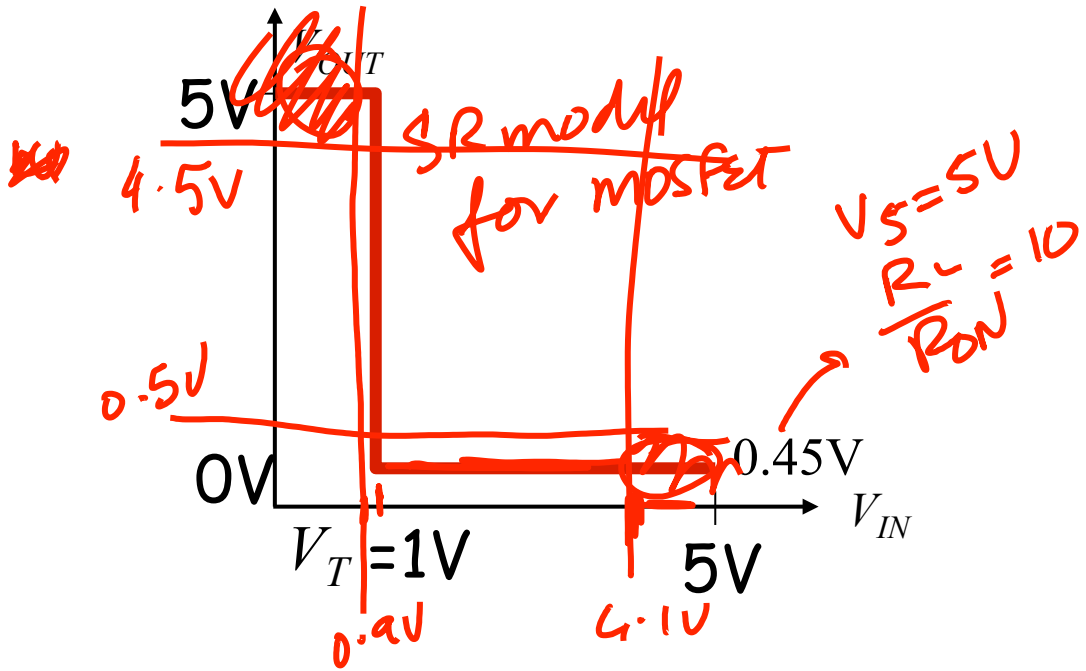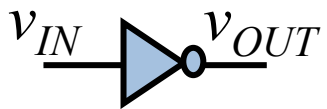Does our inverter satisfy the voltage thresholds for this static discipline?



$V_{OL} = 0.5V$	$V_{IL} = 0.9V$
$V_{OH} = 4.5V$	$V_{IH} = 4.1V$



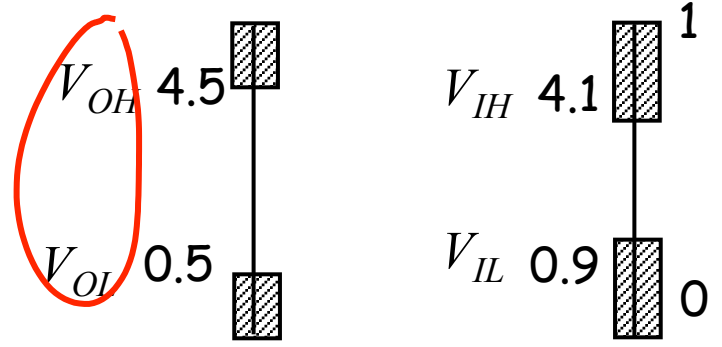


what would happen if you had $\frac{R_L}{R_{ON}} = 5$

So, our inverter satisfies this static discipline


Some Interesting Insights...

Our Digital Subcircuits are Linear

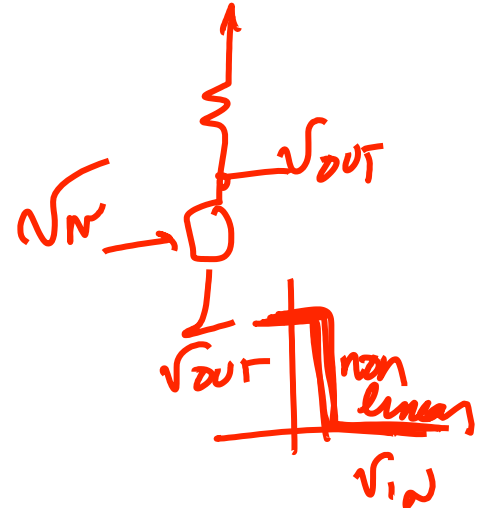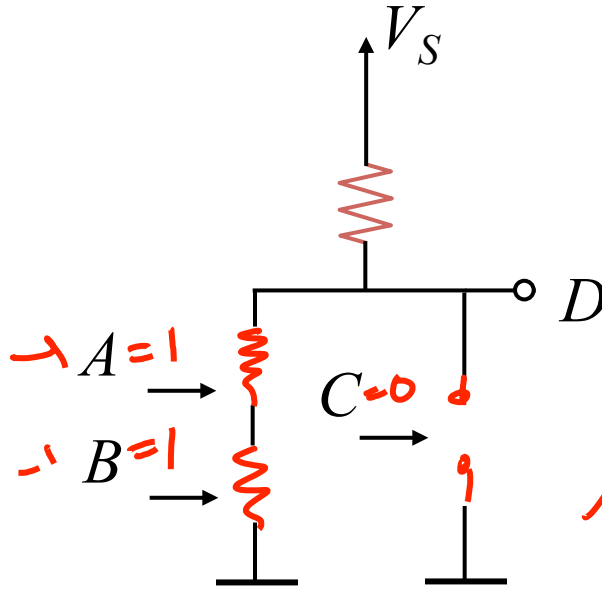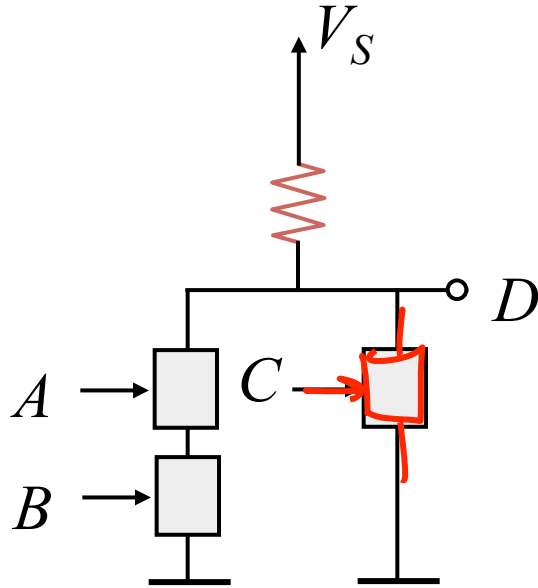


linear subcircuit!

Static Power in Digital Circuits

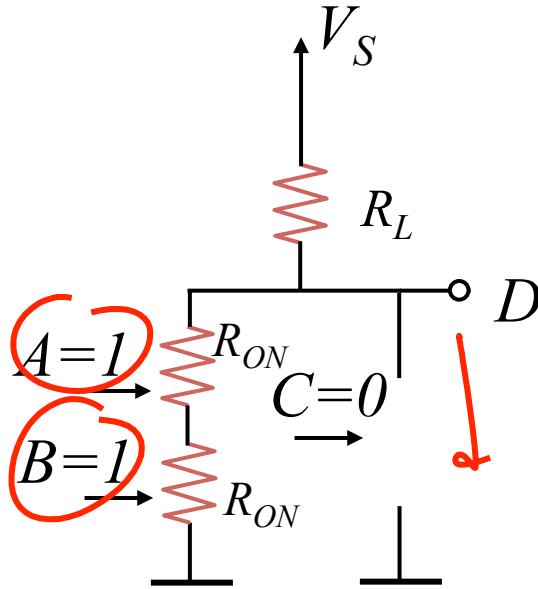

$6.002 \times$

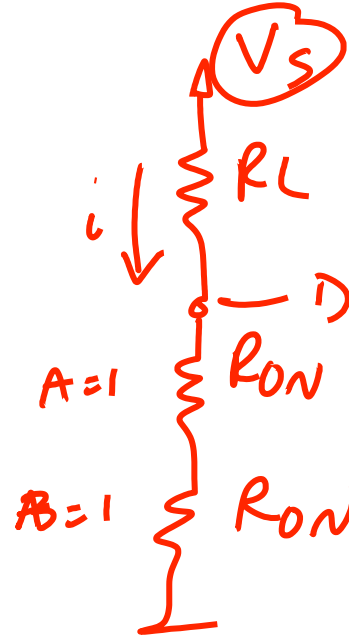

$V_S = 5V$
 $V_T = 1V$

$V_H = 1V$
 $V_S = 5V$
 $V_S = 0.7V$
 $\rightarrow 0.3V - 0.5V$

$$Power = \frac{V_S^2}{2R_{ON} + R_L} = V_S \cdot i$$

$$\frac{V_S}{2R_{ON} + R_L}$$

Analog and Digital (or Mixed Signals) are Everywhere

