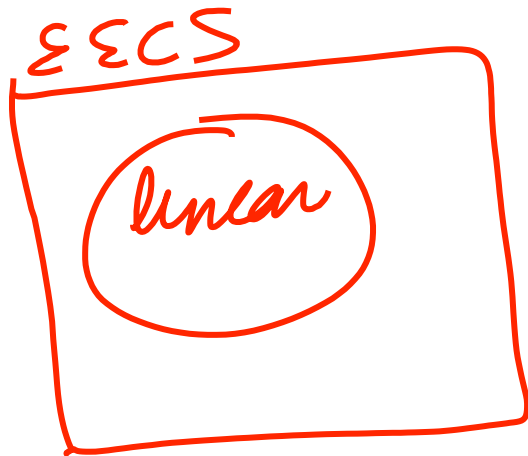


6.002

CIRCUITS AND ELECTRONICS

Superposition,
Thévenin and Norton



Reading: Chapter 3 of A&L



Review

Circuit Analysis Methods

- KVL:

$$\sum_{\text{loop}} V_i = 0$$

- KCL:

$$\sum_{\text{node}} I_i = 0$$


- VI

- ~~Circuit composition rules~~

- Node method - the workhorse of 6.002


KCL at nodes using V 's referenced from ground

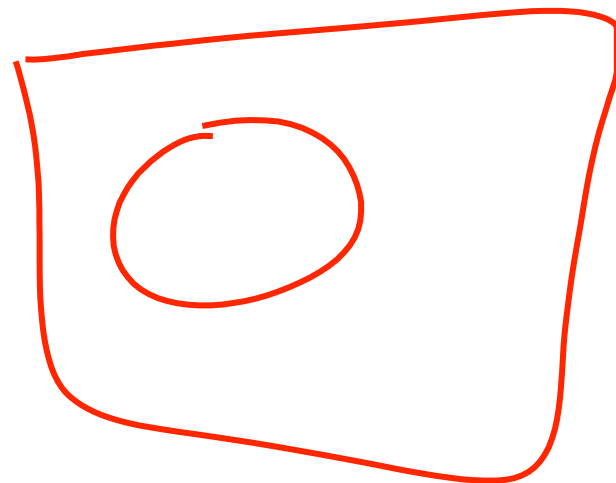KVL implicit in pattern $"(e_i - e_j) \frac{1}{R}"$



Overview

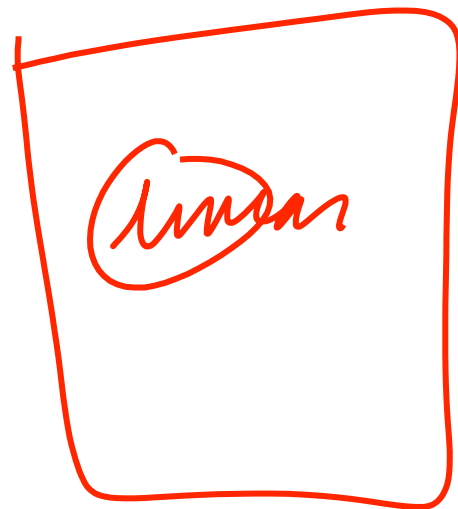
- Introduction to linear circuits
- Properties of linearity
- The superposition tool for your toolkit
- The Thévenin method
- The Norton method



Let's start by introducing linearity

Linearity

Consider

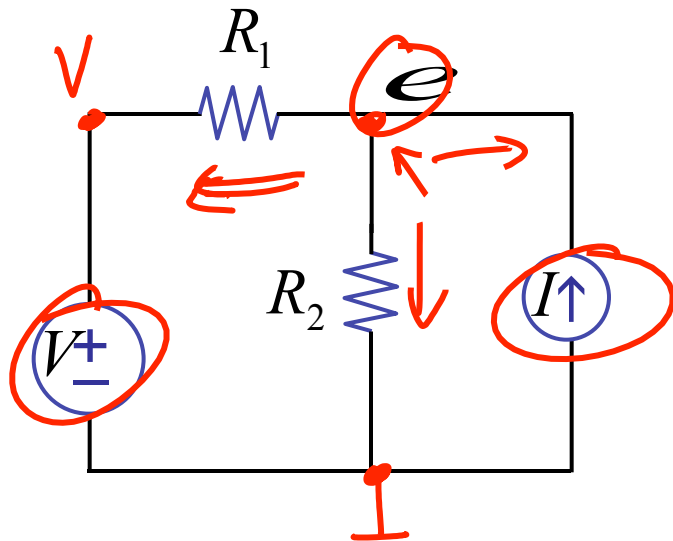

Write node equations -


$$\frac{e - V}{R_1} + \frac{e}{R_2} - I = 0$$

Notice:
linear in
 e, V, I
No terms
 $eV, V^2, VI \dots$

Linearity

Write node equations --
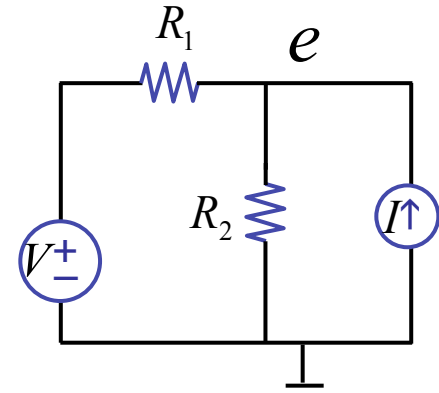
$$\frac{e - V}{R_1} + \frac{e}{R_2} - I = 0 \quad \text{linear in } e, V, I$$




Rearrange --

$$\left[\frac{1}{R_1} + \frac{1}{R_2} \right] e = \frac{V}{R_1} + I$$

Linearity
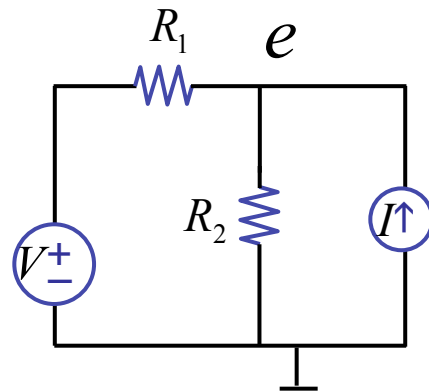
$$\frac{e-V}{R_1} + \frac{e}{R_2} - I = 0$$



$\frac{R_2 + R_1}{R_1 R_2} \left[\frac{1}{R_1} + \frac{1}{R_2} \right] e = \frac{V}{R_1} + I$

conductance matrix G *node voltage* e *linear sum of sources* S

$\rightarrow e = \frac{R_2 V}{R_1 + R_2} + \frac{R_1 R_2 I}{R_1 + R_2}$

linear $\rightarrow e = a_1 V_1 + a_2 V_2 + \dots + b_1 I_1 + b_2 I_2 + \dots$

$G e = S$
 $\begin{bmatrix} \dots \end{bmatrix} \begin{bmatrix} \dots \end{bmatrix} = \begin{bmatrix} \dots \end{bmatrix}$

Linearity



Homogeneity
Superposition

Linearity



Homogeneity
Superposition


Homogeneity



x_1
 x_2
...




y

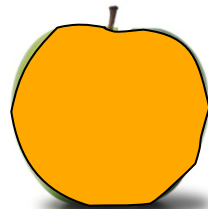

αx_1
 αx_2
...






αy

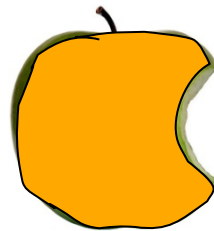


Linearity
Superposition



Homogeneity
Superposition

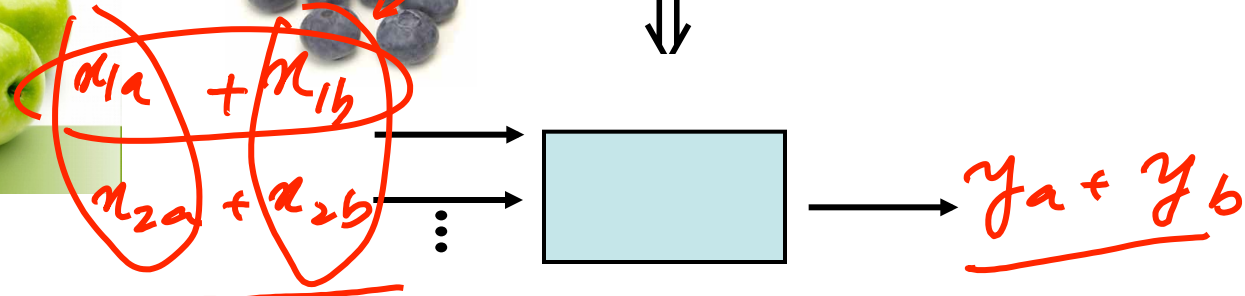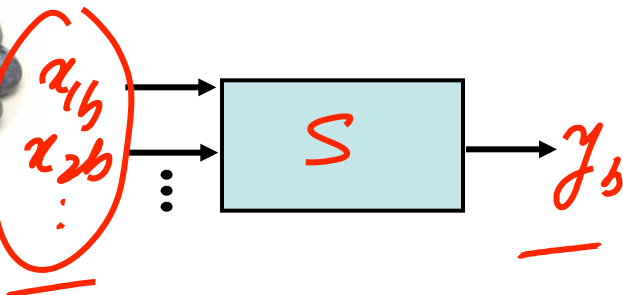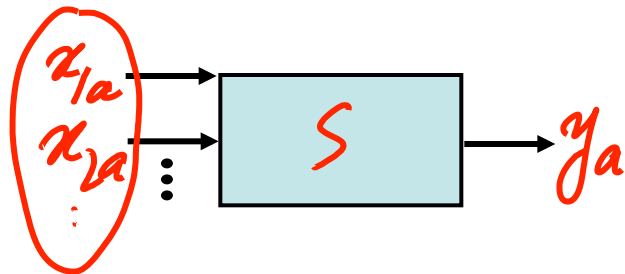


Specific superposition example:

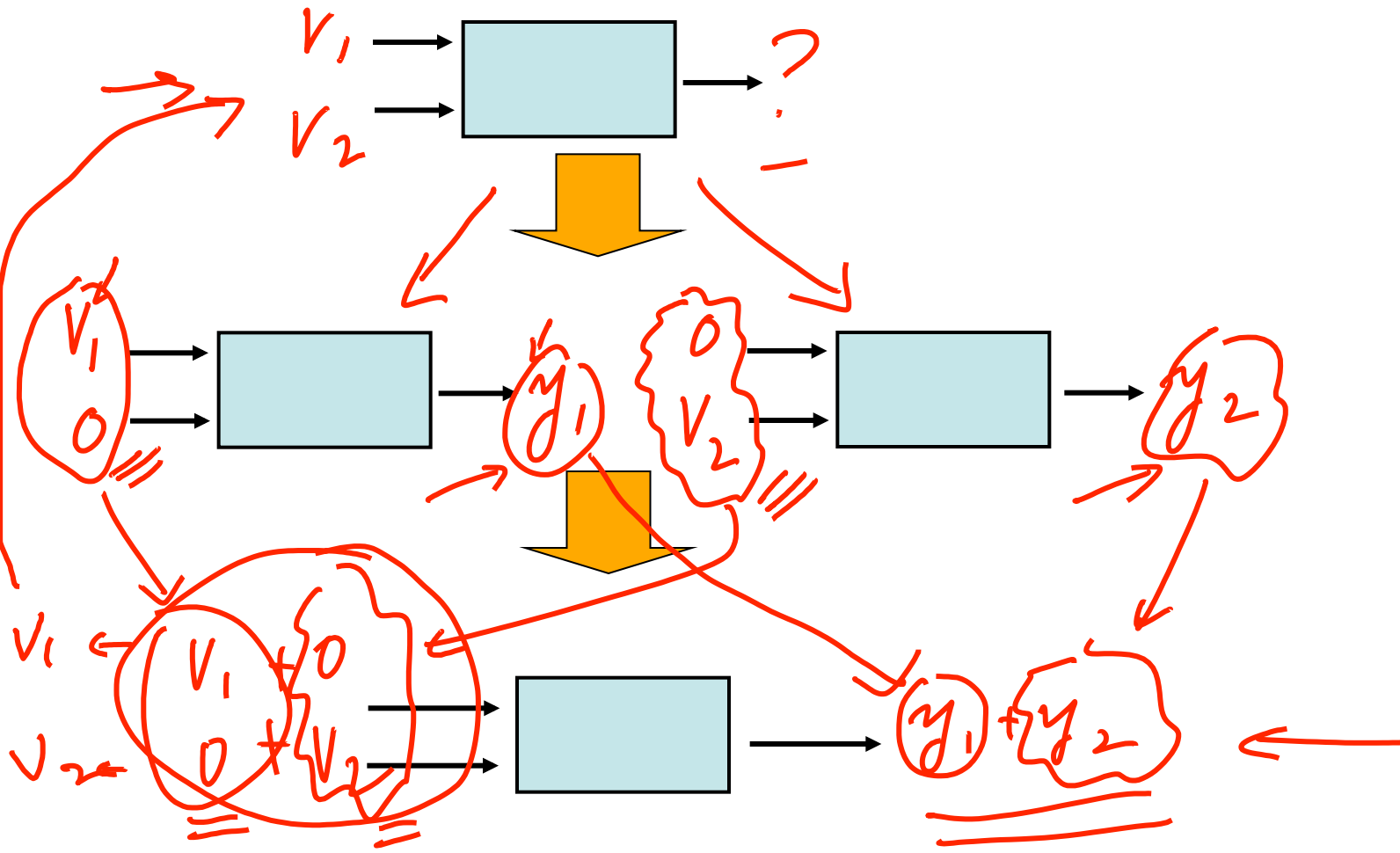

Method 4: Superposition method


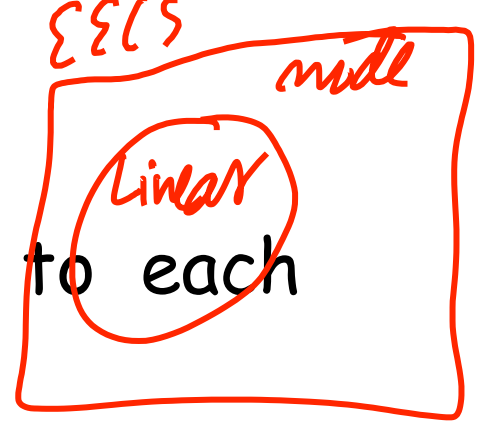
1. Find the responses of the circuit to each source acting alone
2. Sum the individual responses




Independent sources

A red arrow points from the text "Independent sources" to the first step of the superposition method: "Find the responses of the circuit to each source acting alone".

Each source acting alone means this

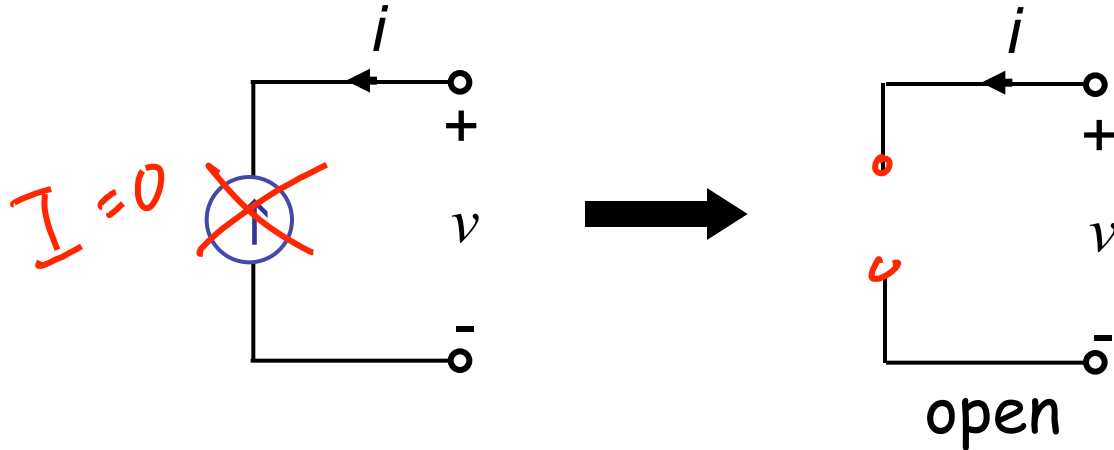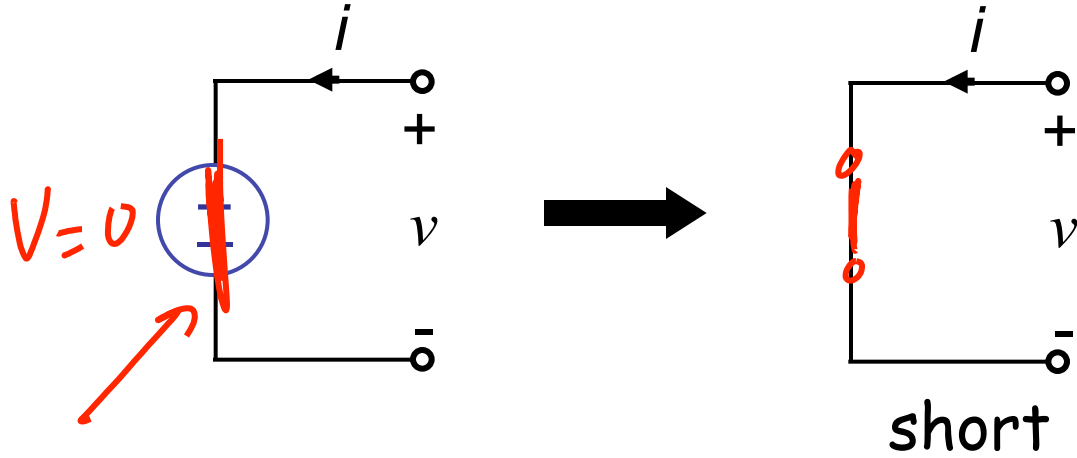

Back to the example

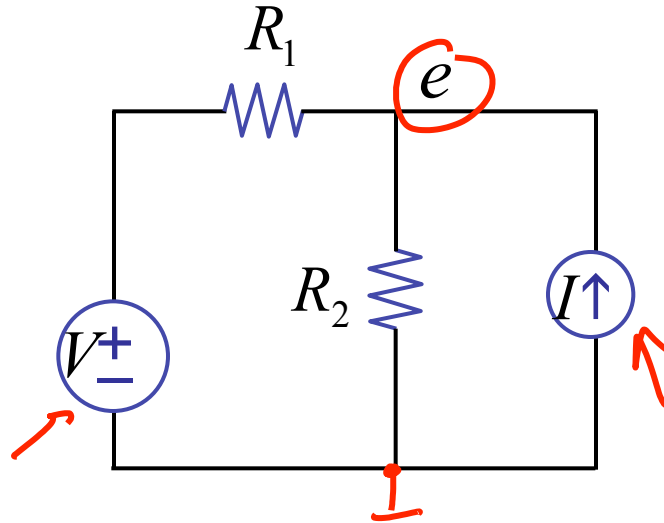



Use superposition method

Back to the example

Use superposition method

1.

V
acting
alone

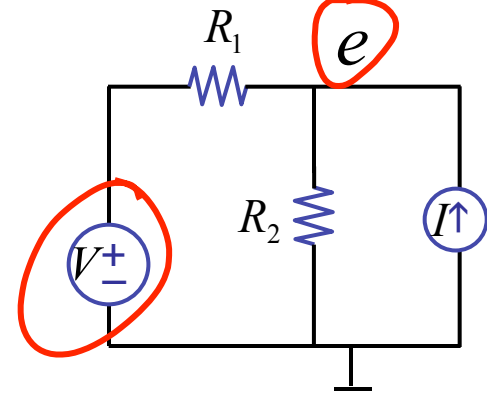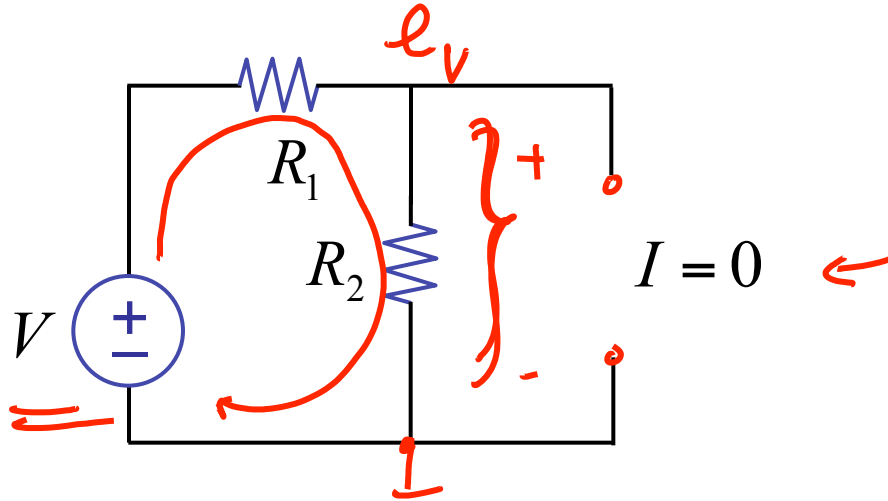


Voltage divider
pattern

$$e_v = \frac{R_2}{R_1 + R_2} V$$

Back to the example

Use superposition method


I
acting
alone

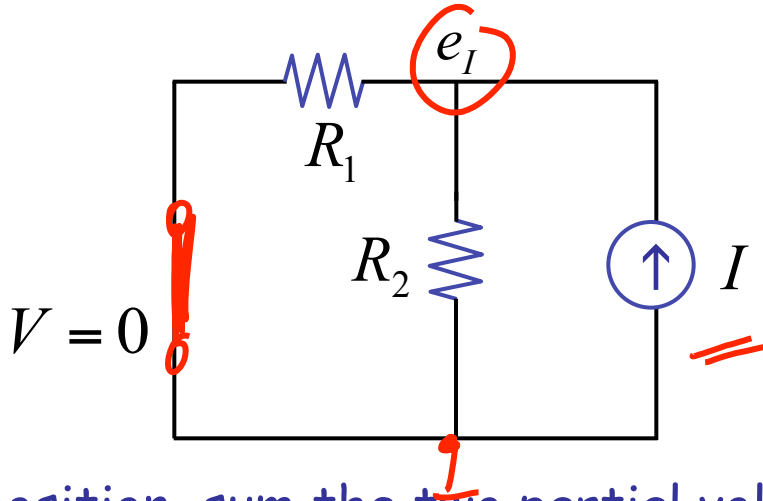

By superposition, sum the two partial voltages

$$e = e_V + e_I = \frac{R_2}{R_1 + R_2} V + \frac{R_1 R_2}{R_1 + R_2} \cdot I$$

$$e_V = \frac{R_2}{R_1 + R_2} V$$

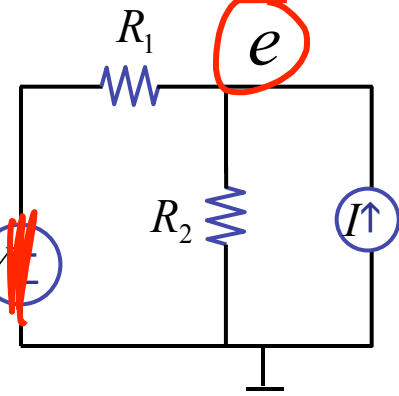


Current flowing
into a resistor
pair in parallel

$$e_I = \frac{R_1 R_2}{R_1 + R_2} \cdot I$$

Voilà!




salt
water

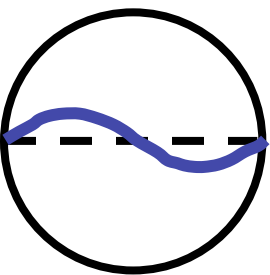



V_1

Low freq
sinusoid

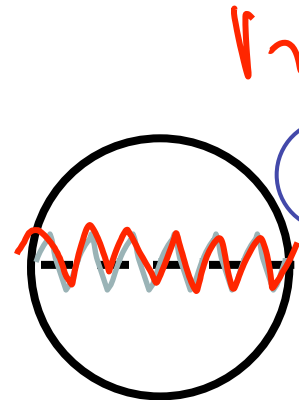

V_2

High freq
triangular wave

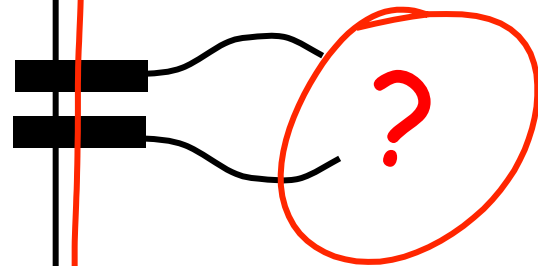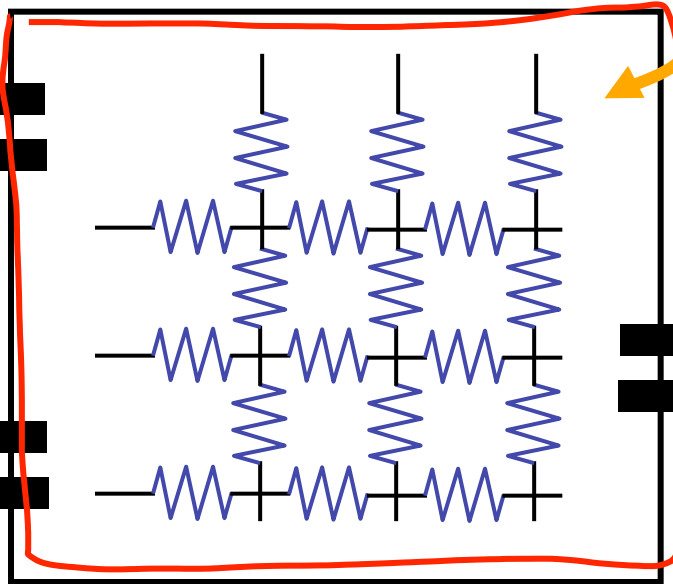


output shows
superposition

$\rightarrow V_1$, $\rightarrow V_2$

Yet another method...

Consider

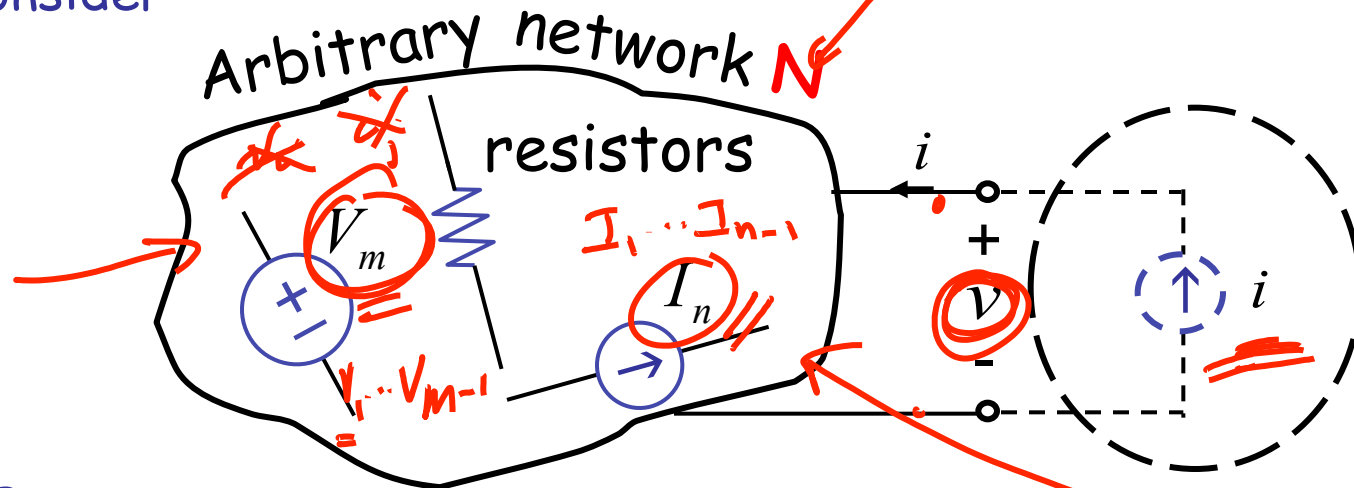

Suppose I want to determine v

By superposition

$$v = \underbrace{\sum_m \alpha_m V_m}_{\text{by setting } I_n = 0} + \underbrace{\sum_n \beta_n I_n}_{\text{by setting } V_m = 0} + \underbrace{R i}_{\text{by setting } V_m = 0, I_n = 0}$$

by setting

$$\forall_n I_n = 0$$


$$i = 0$$

$$\forall_m V_m = 0$$

$$i = 0$$


$$\forall_n I_n = 0$$

$$\forall_m V_m = 0$$

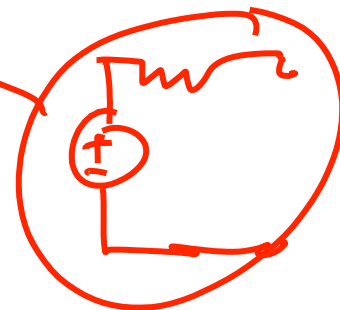

$$v = \sum_m \alpha_m V_m + \sum_n \beta_n I_n + R i$$

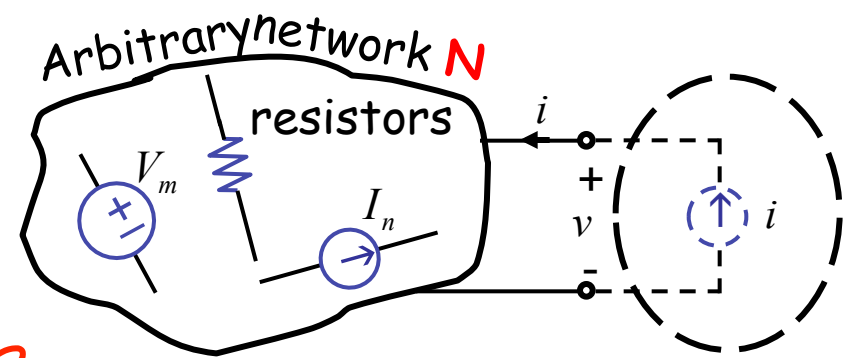α_m : no units
 β_n : Resistance units
 R : Resistance units
 v : voltage




Independent of external excitation and behaves like a voltage.

also independent of external excitement and behaves like a resistor. Let's call it " R_{TH} "


Let's call it " v_{TH} "

$$v = \sum_m \alpha_m V_m + \sum_n \beta_n I_n + Ri$$

$$v = v_{TH} + R_{TH} \cdot i$$

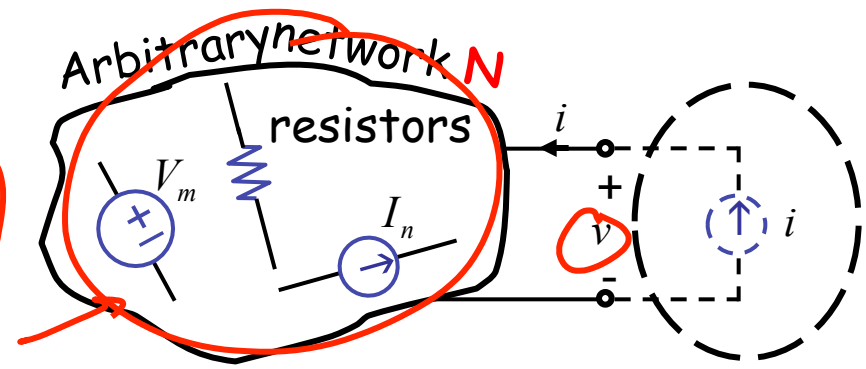


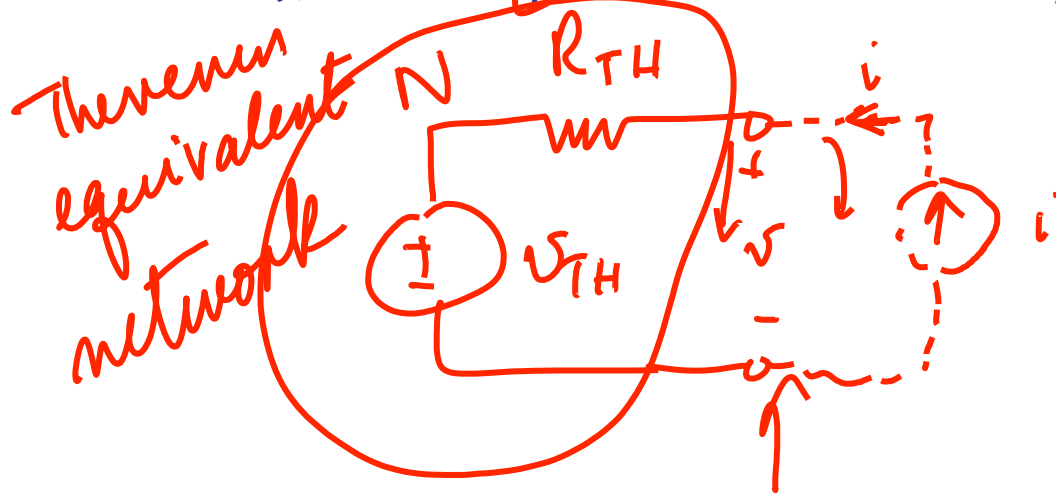
In other words, as far as the external world is concerned (for the purpose of the i - v relation), "arbitrary network N" is indistinguishable from:



Thevenin pattern

$$v = v_{TH} + R_{TH}i$$

Thévenin
equivalent
network

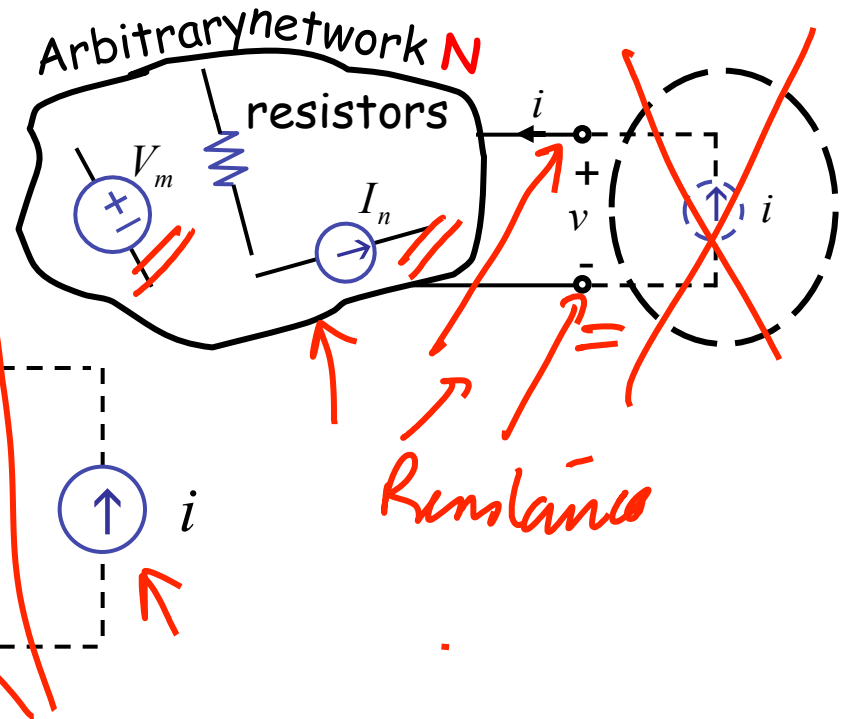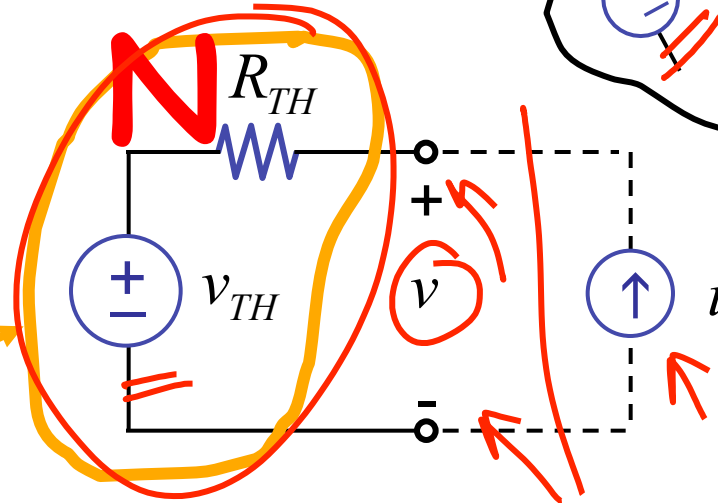

v_{TH}


→ Open circuit voltage seen at terminal pair (aka port)

R_{TH}


→ Resistance of network seen from port

(V_m 's, I_n 's set to 0)

Method 4: The Thévenin Method


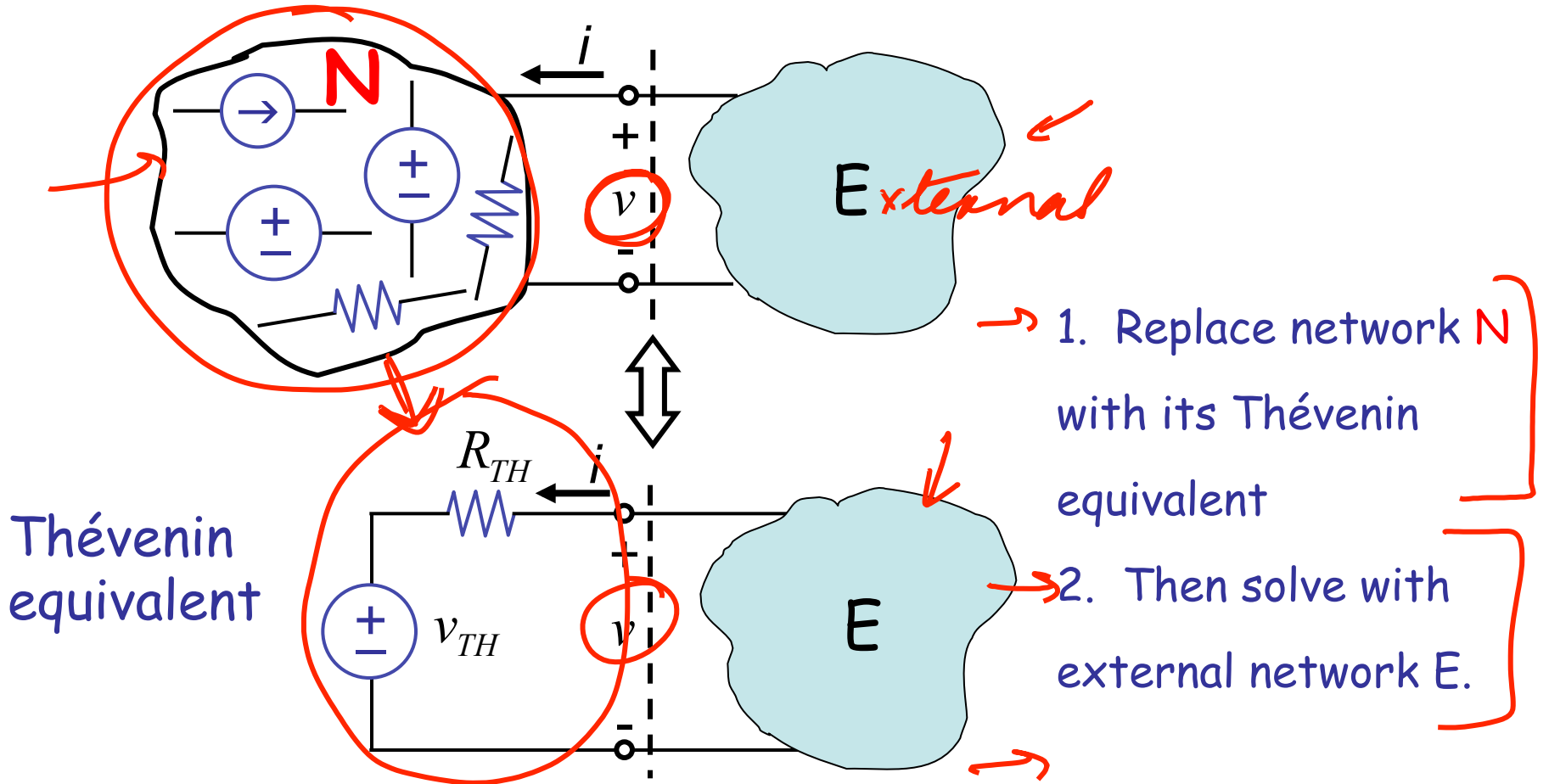


Example: Find i_1

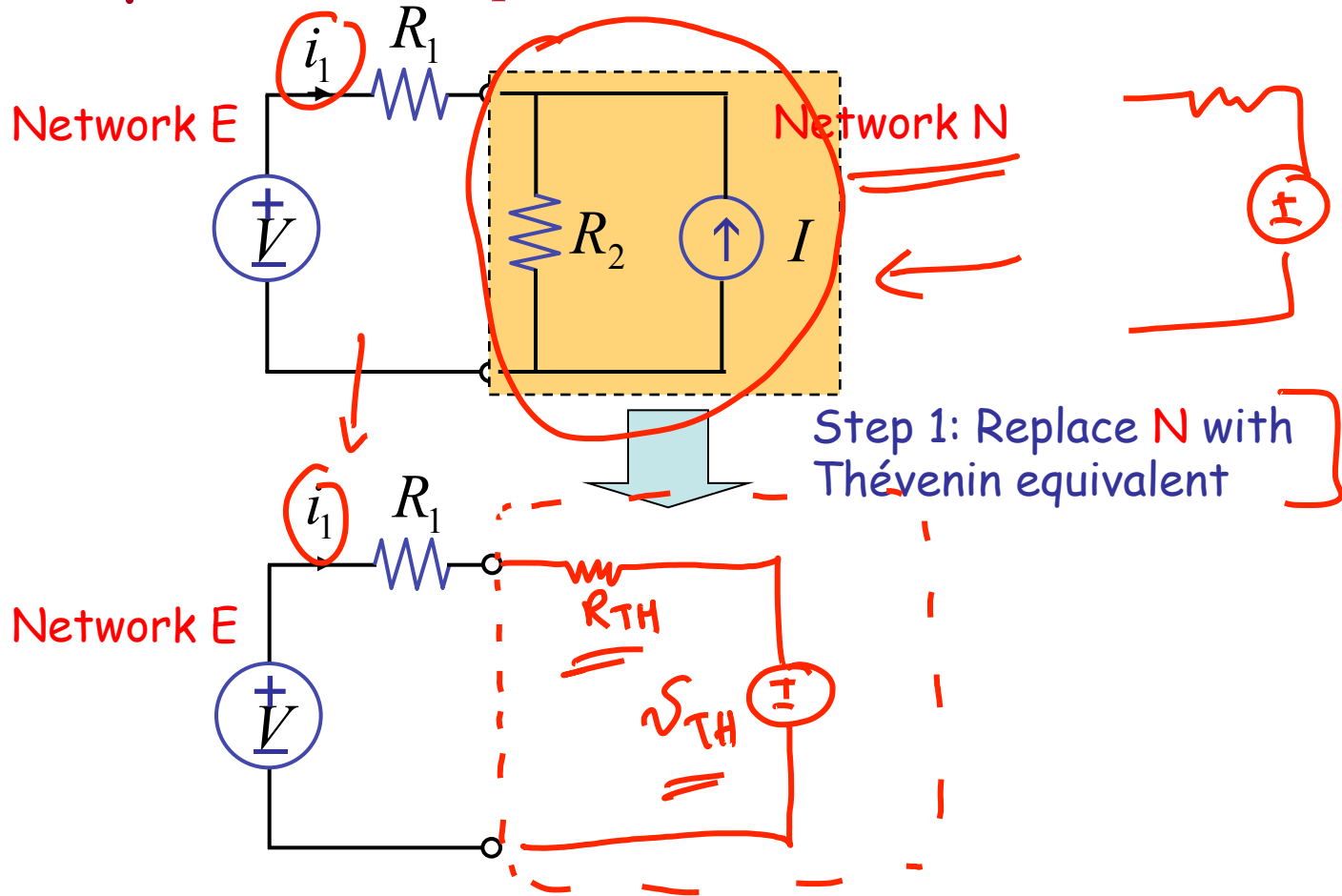



Step 1: Replace with Thévenin equivalent

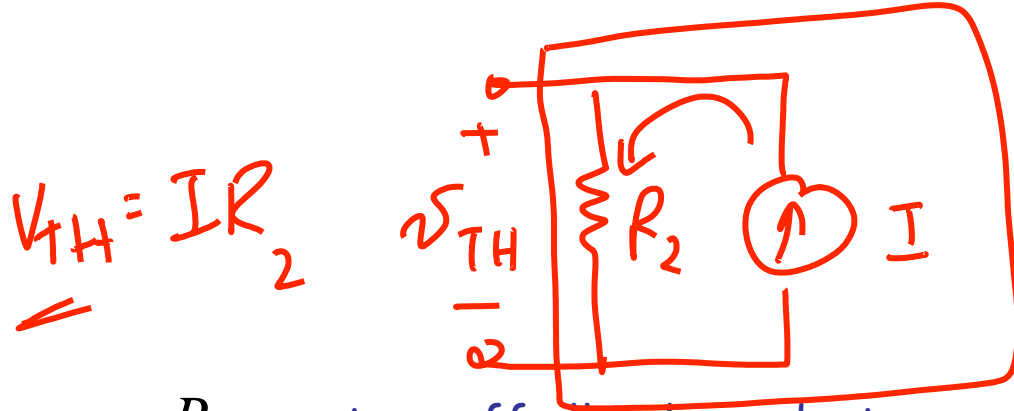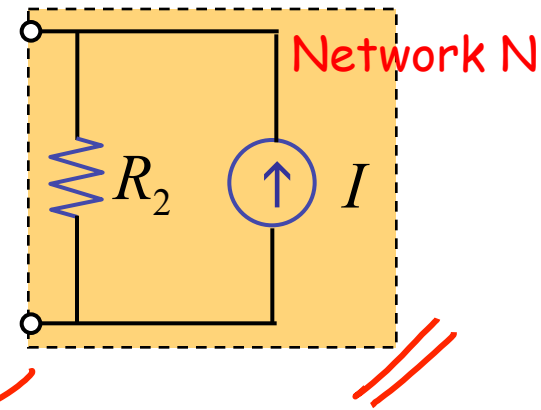V_{TH} : open circuit voltage of network N





$$V_{TH} = IR_2$$

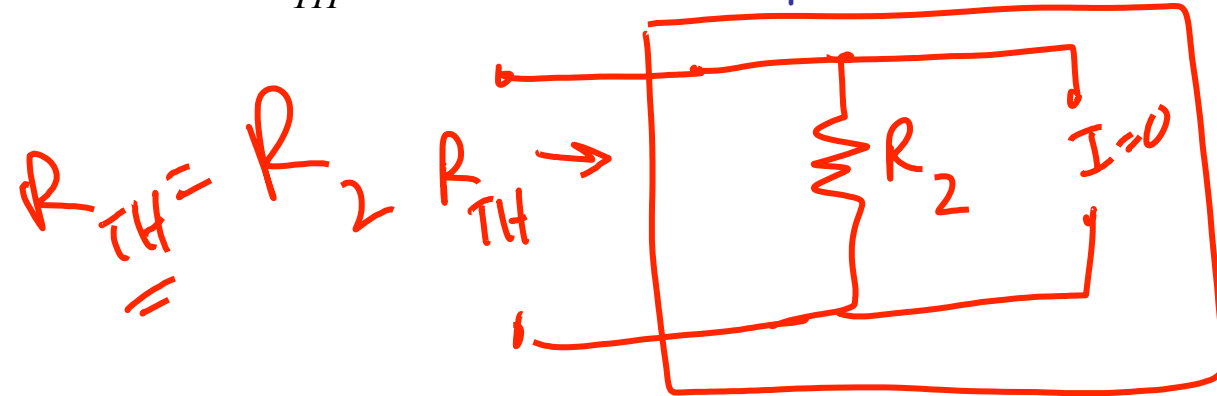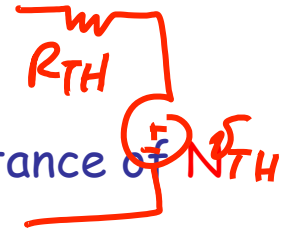R_{TH} : turn off all independent sources and measure resistance of N



$$R_{TH} = R_2$$

Step 2: Solve with external network E

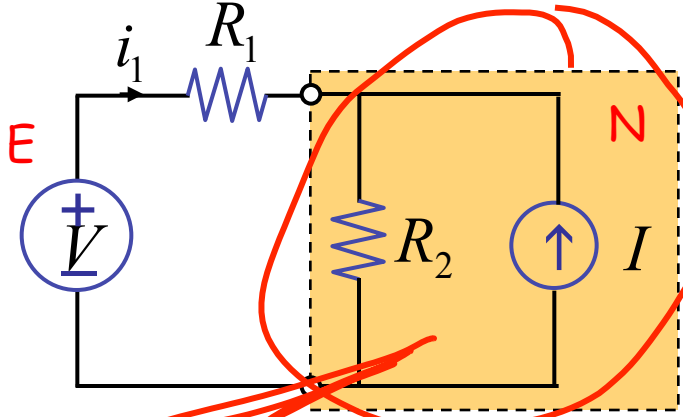
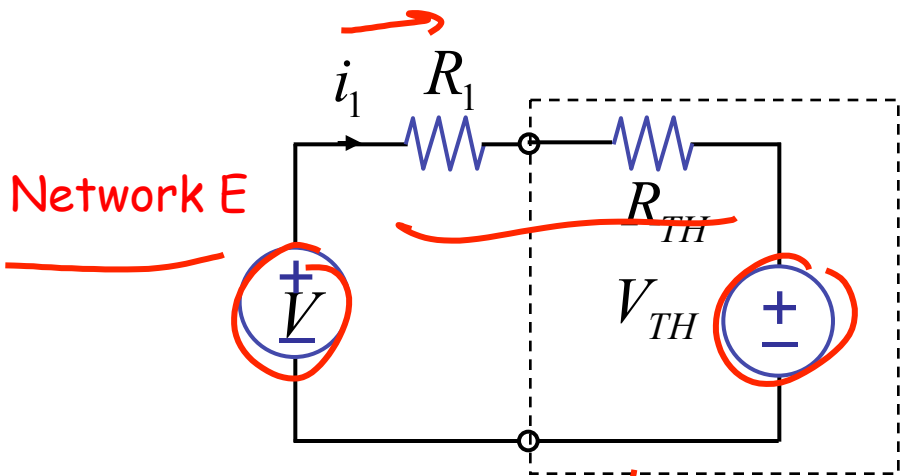


$$\begin{aligned} V_{TH} &= IR_2 \\ R_{TH} &= R_2 \end{aligned}$$

$$i_1 = \frac{V - V_{TH}}{R_1 + R_{TH}}$$

Graphically,

$$v = v_{TH} + R_{TH}i$$

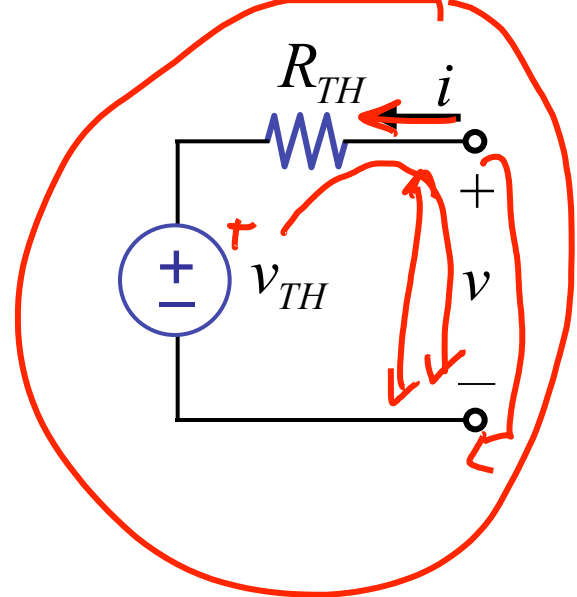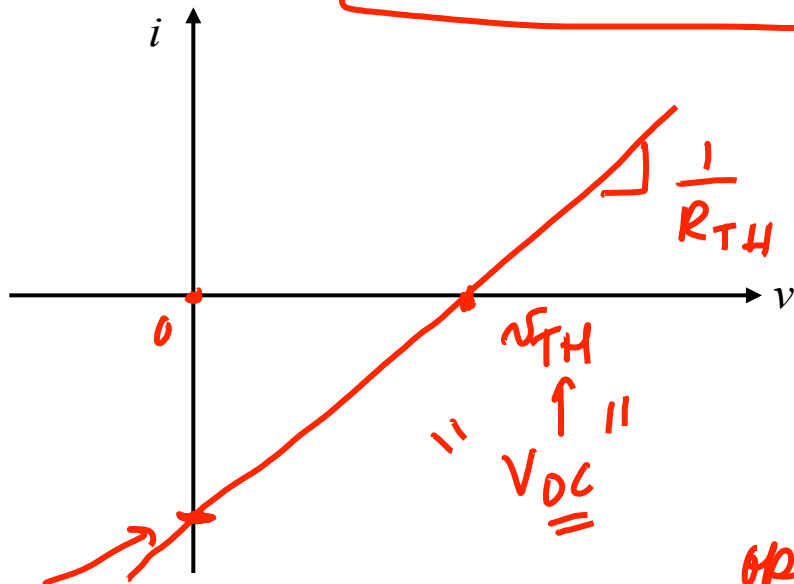

$$I_{SC}$$


open ckt
 $i = 0$

short ckt
 $v = 0$


$$v = v_{TH}$$

$$i = -\frac{v_{TH}}{R_{TH}}$$



Method 5: The Norton Method

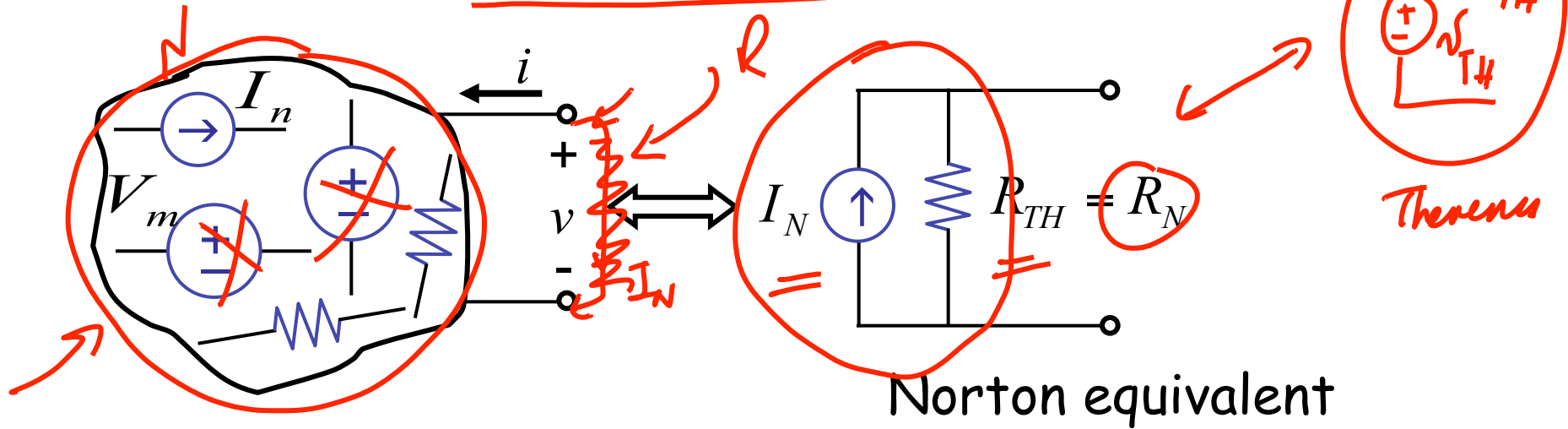

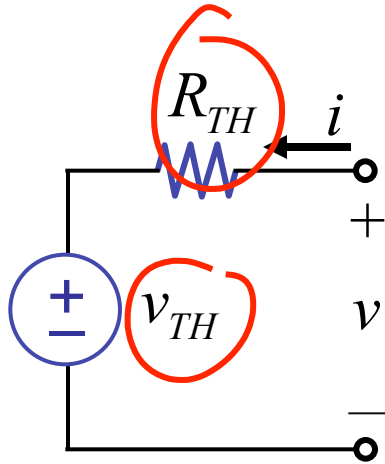- I_N \longrightarrow Short circuit current seen at port
 $R_{TH} = R_N$ \longrightarrow Resistance of network seen from port
 (V'_m 's, I'_n 's set to 0)



Thevenin equivalent

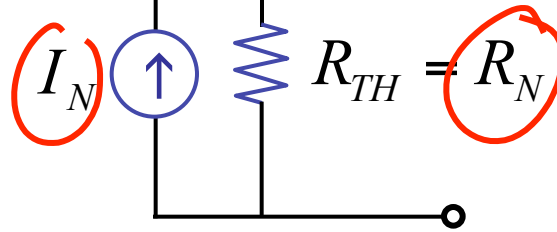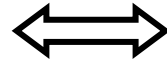


Norton equivalent

$$R_{TH} = R_N$$

$$I_N = \frac{V_{TH}}{R_{TH}}$$

Summary

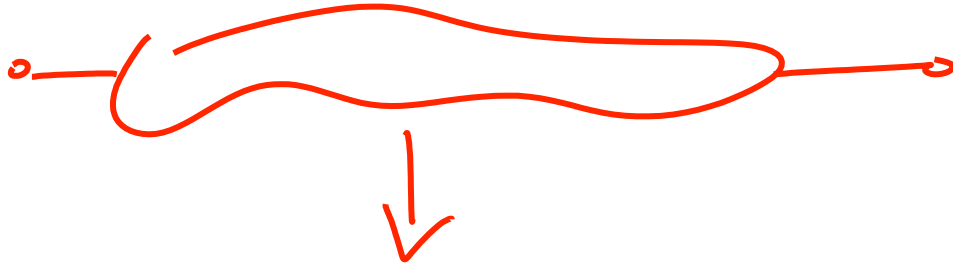Discretize matter by agreeing to observe the lumped matter discipline



Lumped circuit abstraction

Summary

Circuit analysis methods

KVL, KCL, I – V –
Combination rules –

Node method

Superposition

Thévenin

Norton

any network

linear networks

Next – Nonlinear networks