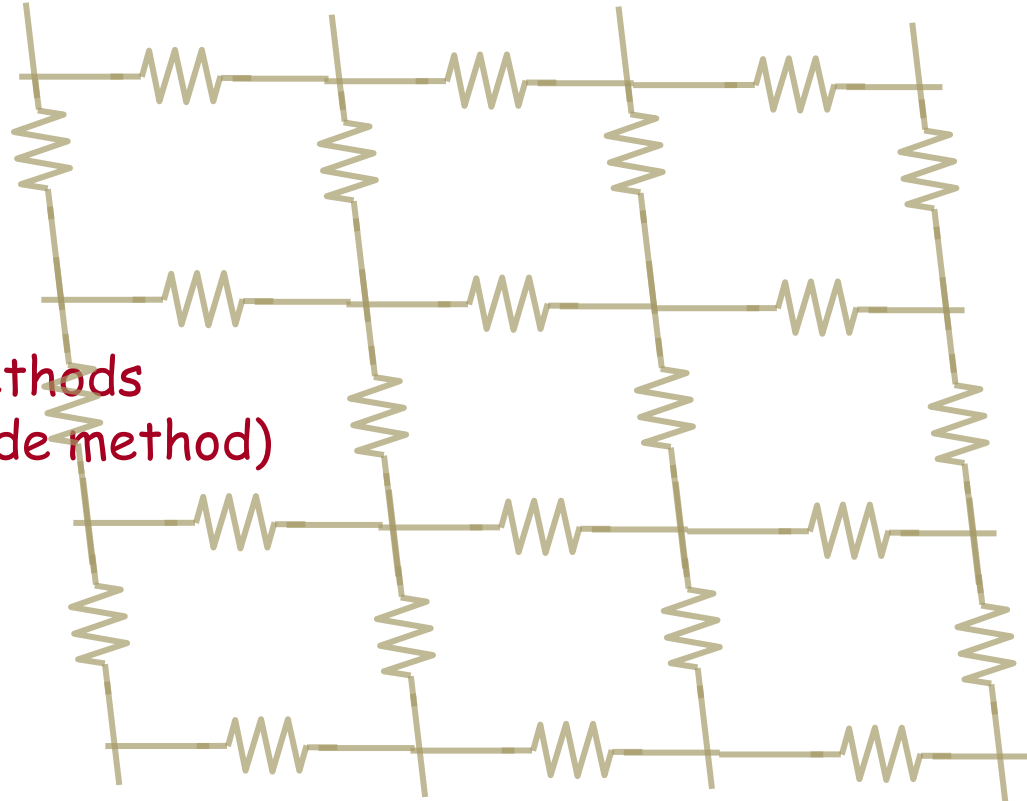


6.002x

CIRCUITS AND ELECTRONICS

Basic Circuit Analysis Methods
(KVL and KCL method, Node method)




Review

Remember, our EECS playground

Observe the lumped
matter discipline LMD



Review

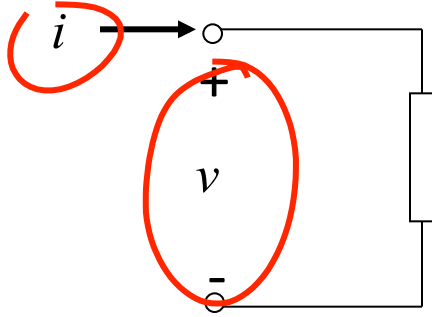


Lumped circuit element

power consumed by element $\neq vi$

Review

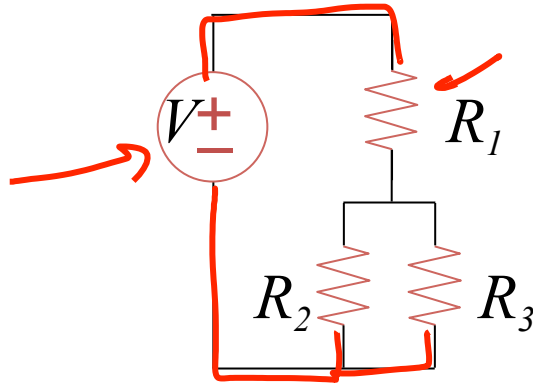LMD allows us to create the lumped circuit abstraction



Review

Maxwell's equations simplify to algebraic KVL and KCL under LMD!

KVL:


$$\sum_j v_j = 0$$

For all loops

KCL:

$$\sum_j i_j = 0$$

For all nodes

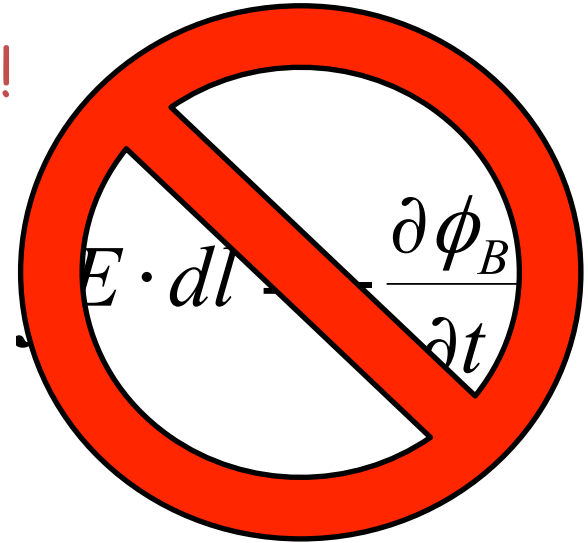

Review


$$i_{ca} + i_{da} + i_{ba} = 0$$

KCL

DEMO

KVL


$$v_{ca} + v_{ab} + v_{bc} = 0$$

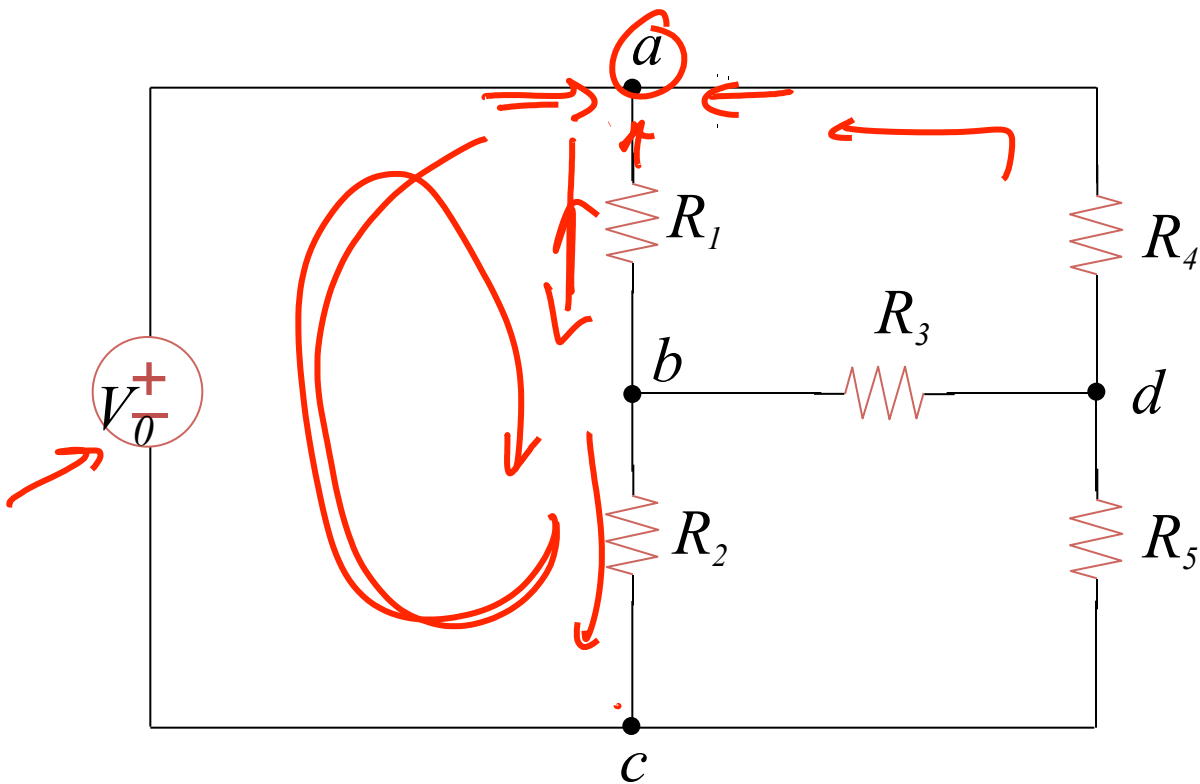

Let's Begin by Building a Toolchest of Analysis Techniques

Analyzing a circuit means:

Find all the element v 's and i 's

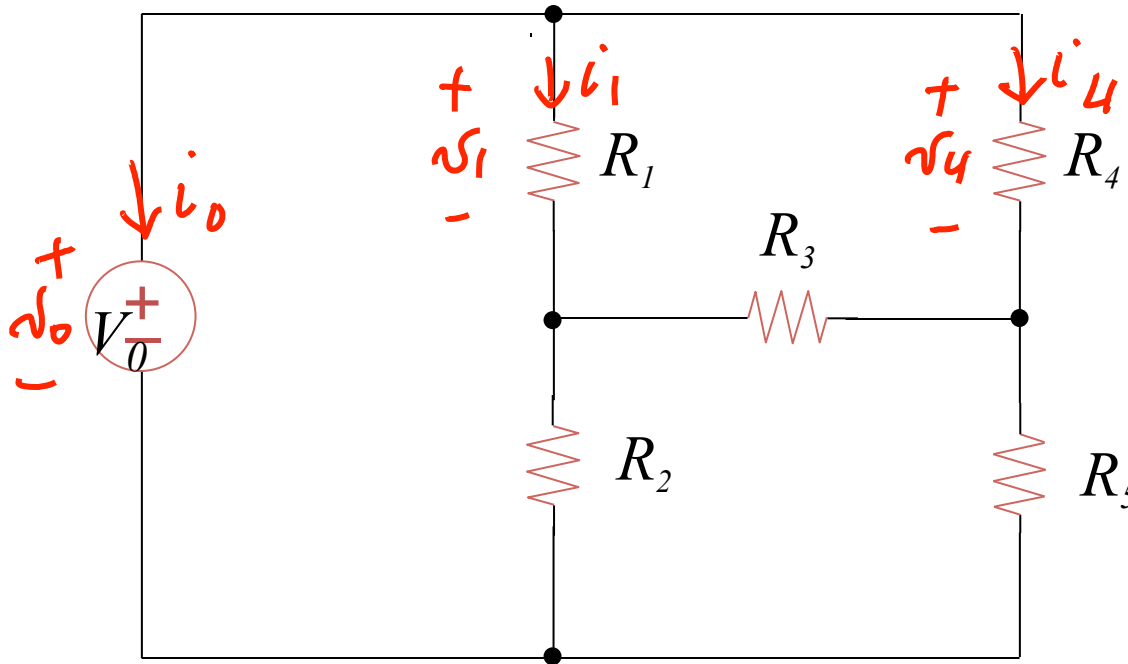

Method 1: Basic KVL, KCL method of Circuit analysis

Goal: Find all element v's and i's


1. write element v-i relationships
(from lumped circuit abstraction)
2. write KCL for all nodes
3. write KVL for all loops

lots of unknowns
lots of equations
lots of fun
solve

Method 1: Basic KVL, KCL method of Circuit analysis

Goal: Find all element v 's and i 's

Labeling element v 's and i 's

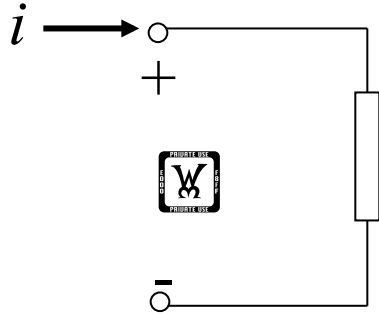

Element e

**This
convention is
called:
Associated
variables
discipline**

Current is taken to be positive going into the positive voltage terminal


Then power consumed by element e

$$\left. \begin{array}{l} \text{Current is taken to be positive going into the positive voltage terminal} \\ \text{Then power consumed by element } e \end{array} \right\} = \mathbf{vi} \text{ is positive}$$


Method 1: Basic KVL, KCL method of Circuit analysis

You will need this for step 1: Element Relationships


For R

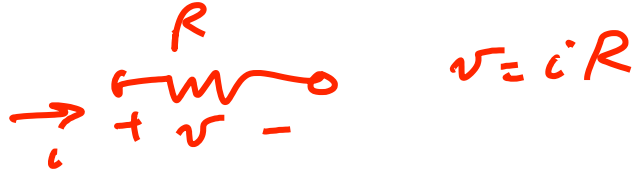

For voltage source

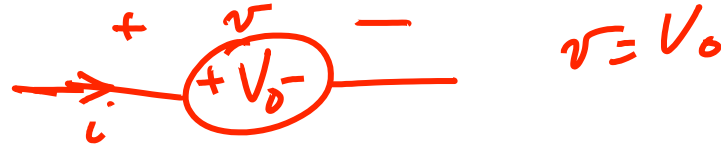


For current source

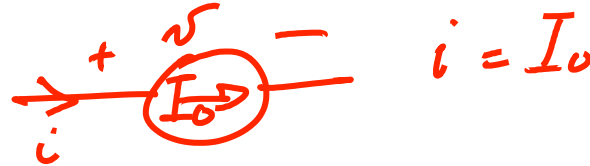

Let's Apply KVL, KCL Method to this Example

Goal: Find all element v's and i's

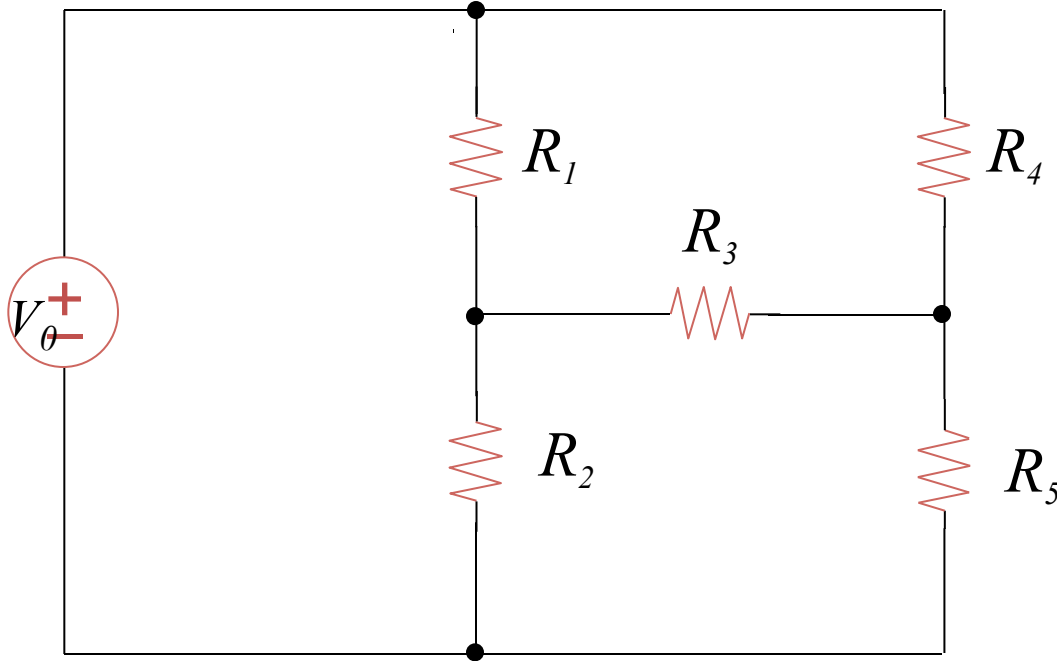


The Demo Circuit

KVL, KCL Example

Label all v's and i's

Goal: Find all element v's and i's

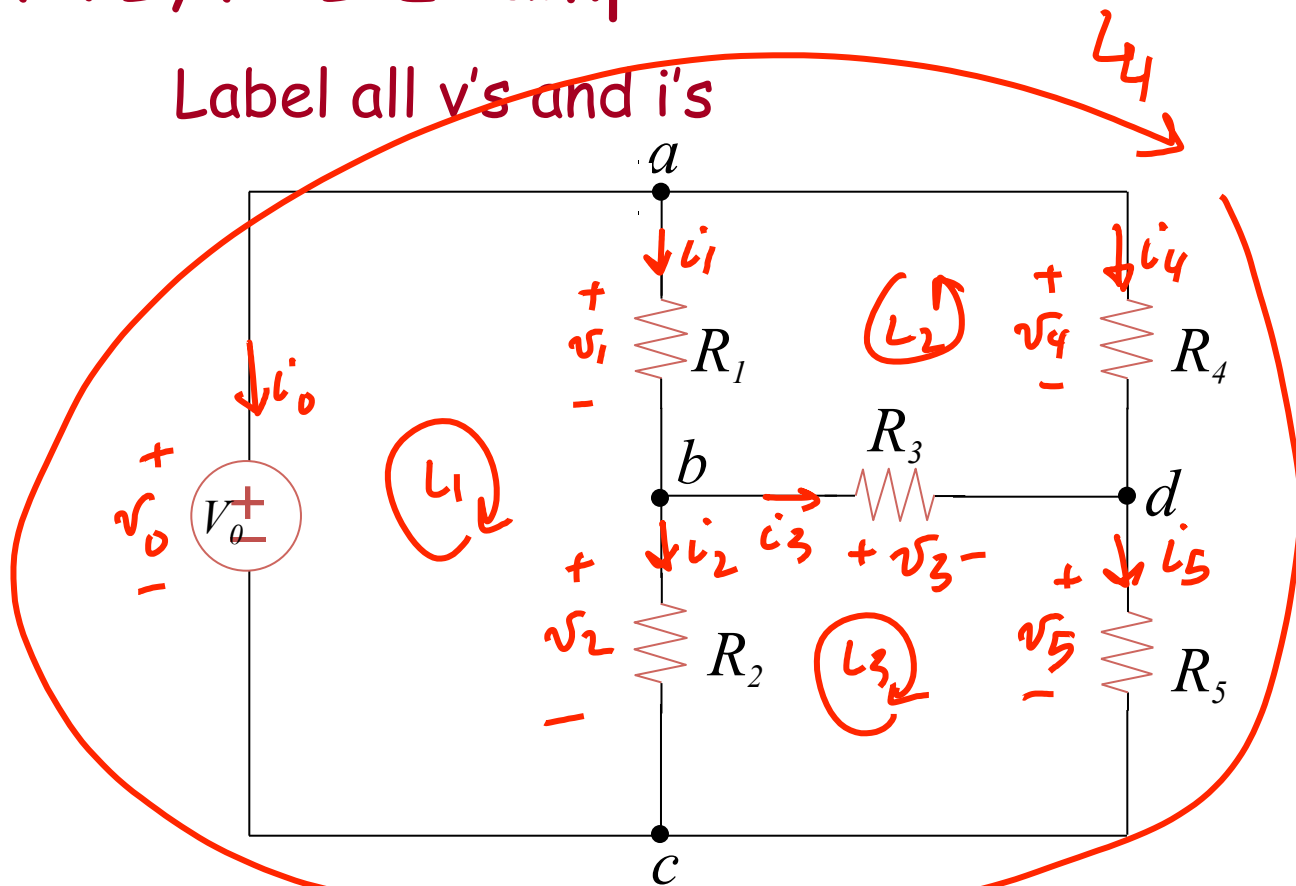

12 unknowns
 $v_0 \dots v_5, i_0 \dots i_5$

Note the use of associated variables...


Step 1 of KVL, KCL Method

$v_0 \dots v_5, i_0 \dots i_5$ 12 unknowns

1. Element relationships (v, i)


$$\begin{aligned} v_0 &= V_0 \leftarrow \text{given} & v_3 &= i_3 R_3 \\ v_1 &= i_1 R_1 & v_4 &= i_4 R_4 \\ v_2 &= i_2 R_2 & v_5 &= i_5 R_5 \end{aligned}$$

6 equations

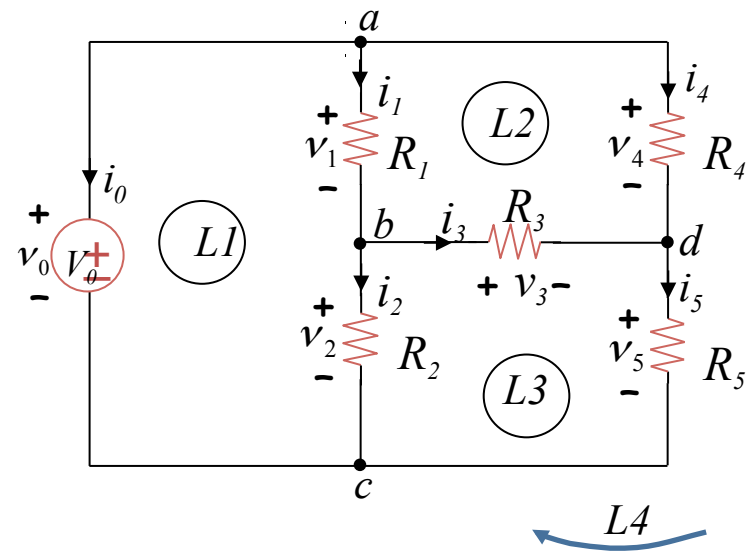

Step 2 of KVL, KCL Method

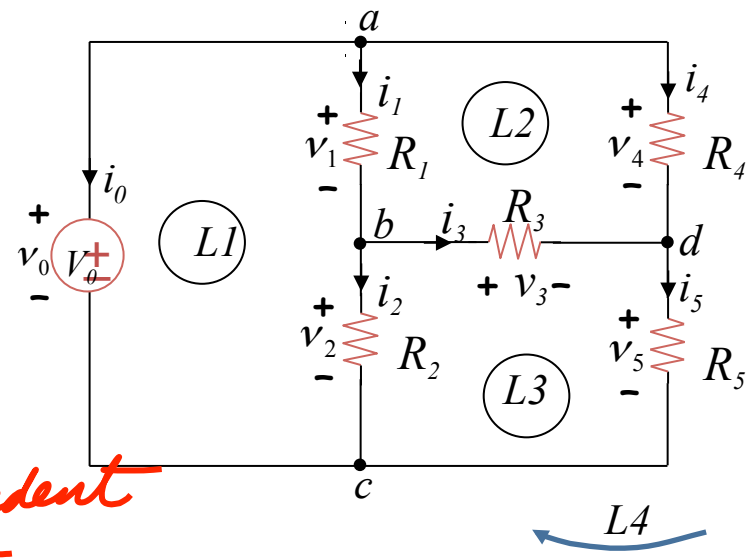$v_0 \dots v_5, i_0 \dots i_5$ 12 unknowns



2. KCL at the nodes

$$a: i_0 + i_1 + i_4 = 0$$

$$b: i_2 + i_3 - i_1 = 0$$


$$d: i_5 - i_3 - i_4 = 0$$

$$c: -i_0 - i_2 - i_5 = 0 \text{ redundant (use convention, e.g., sum currents leaving the node)}$$

3 independent equations

Step 3 of KVL, KCL Method

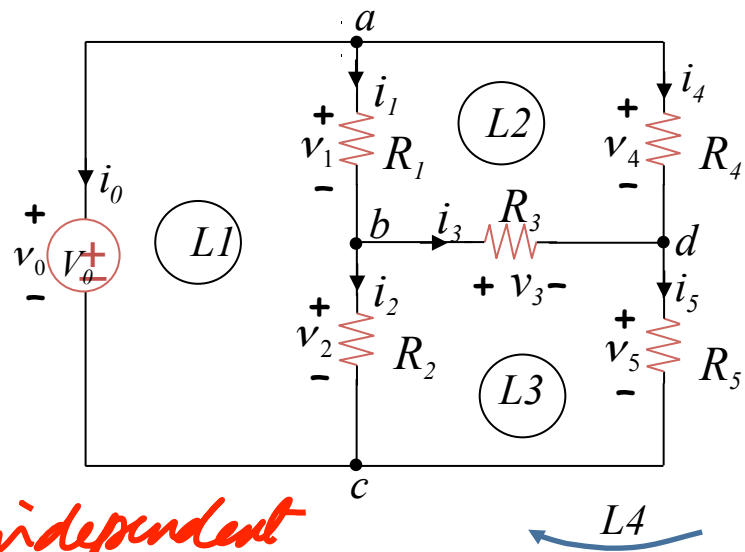$v_0 \dots v_5, i_0 \dots i_5$ 12 unknowns



3. KVL for loops

$$L1: -v_0 + v_1 + v_2 = 0$$

$$L2: +v_1 + v_3 - v_4 = 0$$

$$L3: v_3 + v_5 - v_2 = 0$$

$$L4: -v_0 + v_4 + v_5 = 0 \text{ redundant}$$

3 independent equations

(use convention, e.g., as you go around loop, assign first encountered sign to each voltage)

KVL, KCL Method

1. Element v, i relationships

$$\begin{array}{ll} v_0 = V_0 & v_3 = i_3 R_3 \\ v_1 = i_1 R_1 & v_4 = i_4 R_4 \\ v_2 = i_2 R_2 & v_5 = i_5 R_5 \end{array}$$

6

3. KVL for loops

$$L1: -v_0 + v_1 + v_2 = 0$$

$$L2: v_1 + v_3 - v_4 = 0$$

$$L3: v_3 + v_5 - v_2 = 0$$

$$L4: -v_0 + v_4 + v_5 = 0 \text{ redundant}$$

3

2. KCL at the nodes


$$a: i_0 + i_1 + i_4 = 0$$

$$b: i_2 + i_3 - i_1 = 0$$

$$d: i_5 - i_3 - i_4 = 0$$

$$c: -i_0 - i_2 - i_5 = 0 \text{ redundant}$$



3

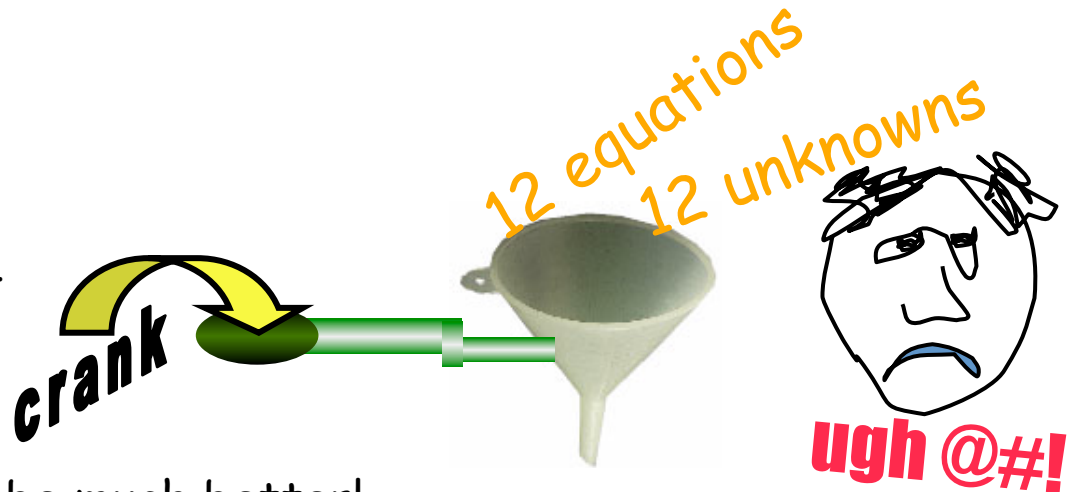

Method 3 - the node method will be much better!


Other Analysis Methods

Method 2— Apply element combination rules

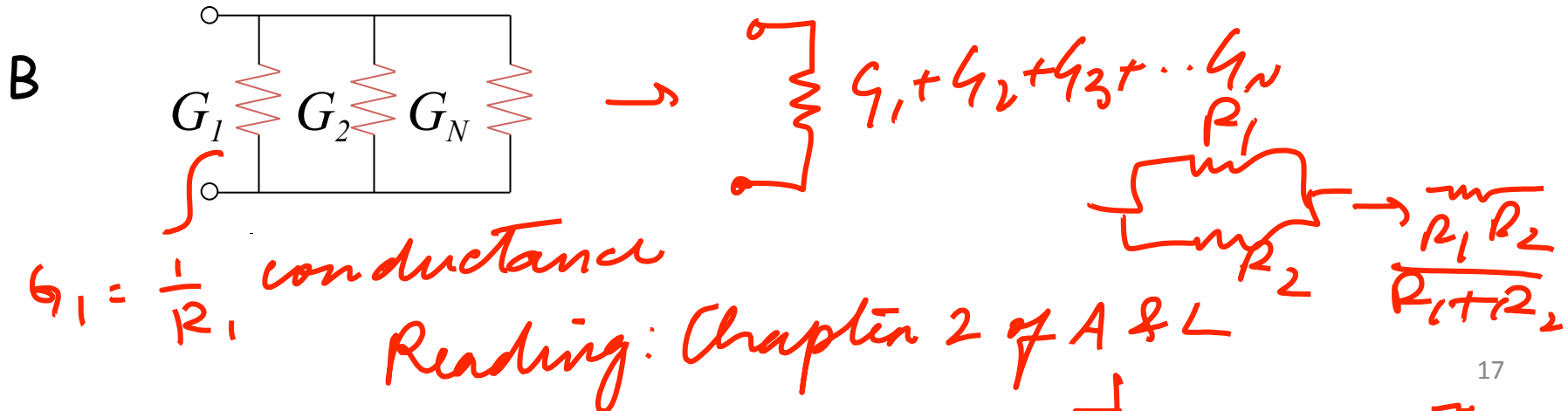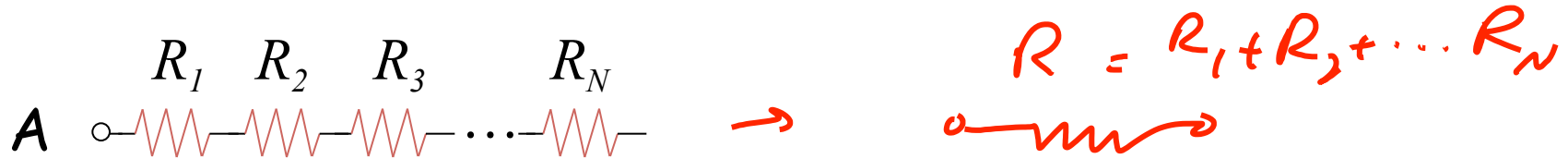


Method 2 — Apply element combination rules

C

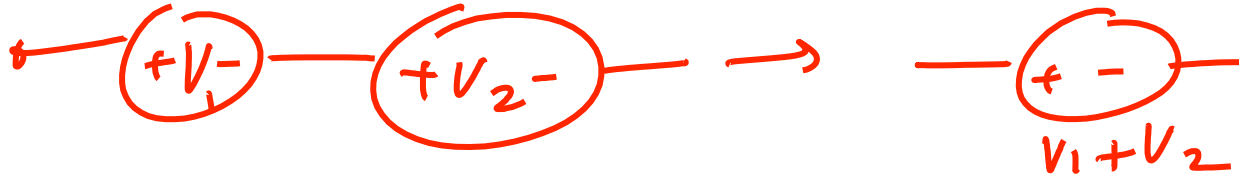


D

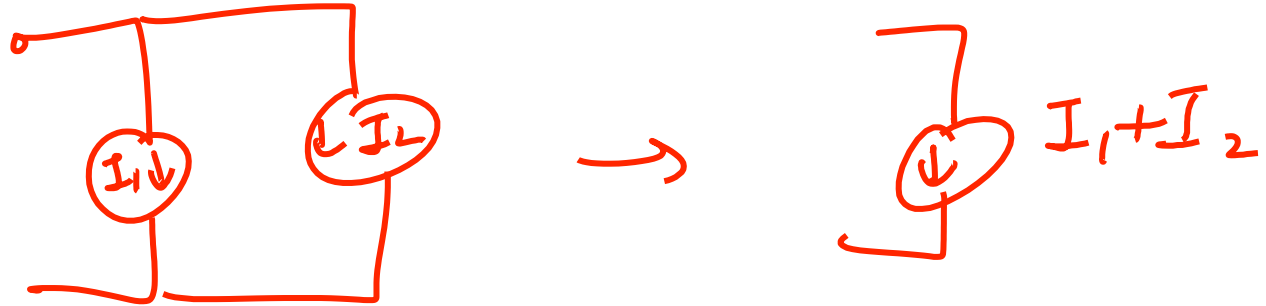

Method 2— Apply element combination rules

Example

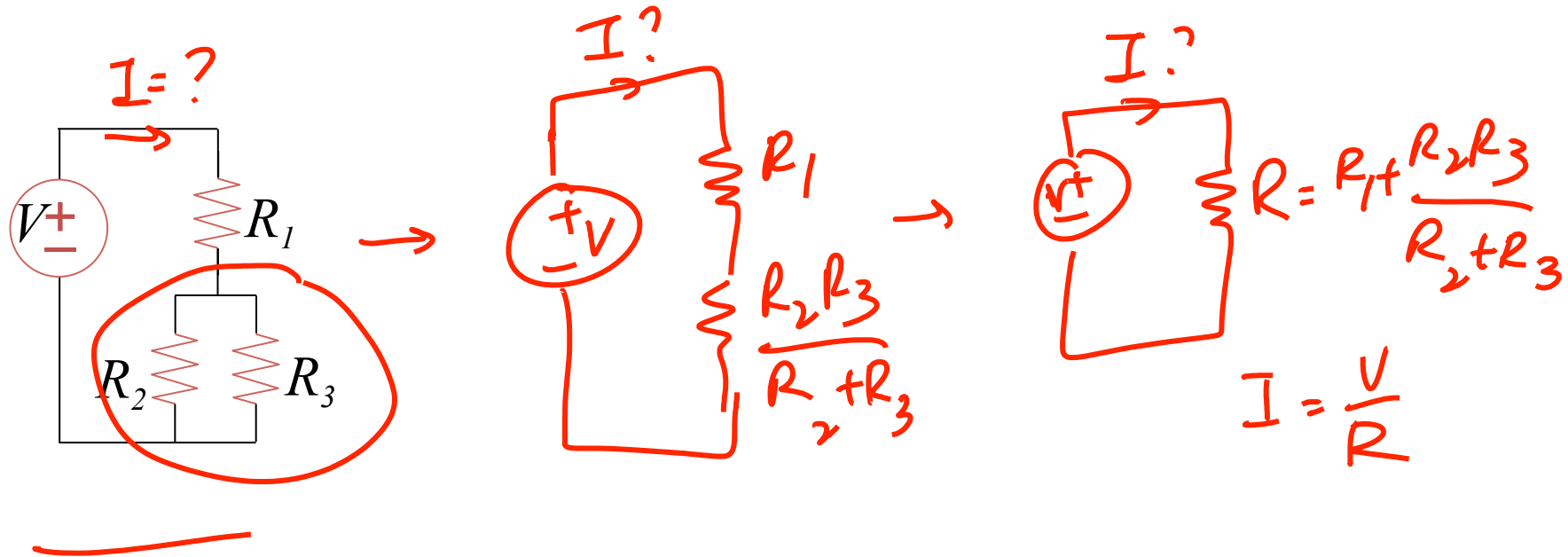

Method 3 — Node analysis

1. Select reference node (↓ ground) from which voltages are measured.
2. Label voltages of remaining nodes with respect to ground. These are the primary unknowns.
3. Write KCL for all but the ground node, substituting device laws and KVL.
--
4. Solve for node voltages.
5. Back solve for branch voltages and currents (i.e., the secondary unknowns).


Particular
application of
KVL, KCL
method



6.002x
workhorse!

Method 3 — Node analysis

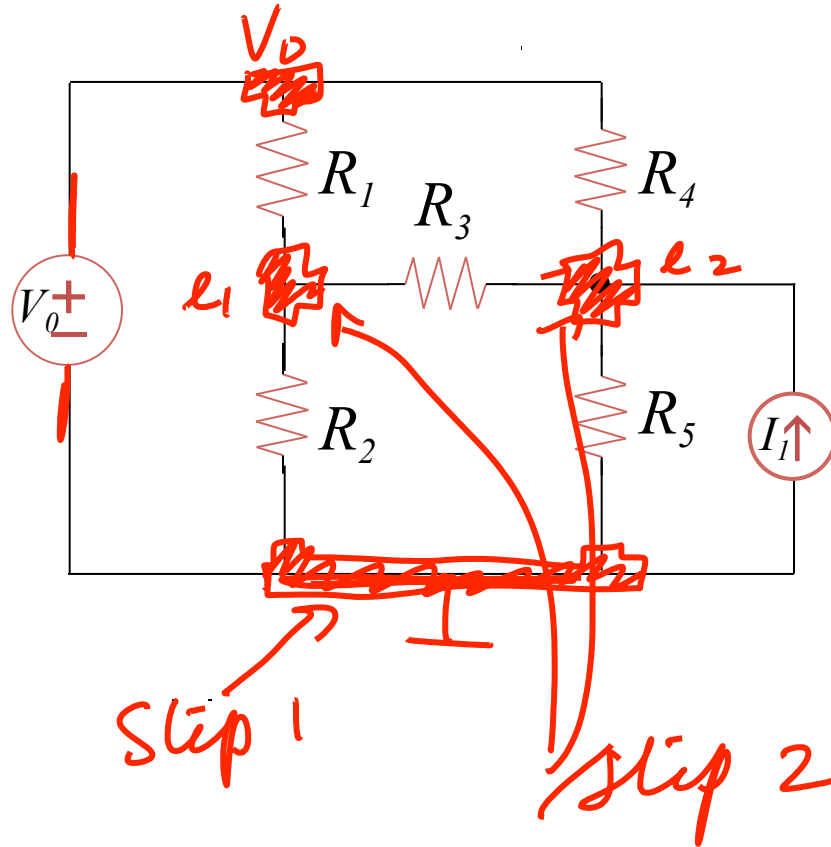Example: Old Faithful, plus current source



1. Select reference ground node
2. Label node voltages with respect to ground.

Step 3 of Node Method

For convenience, write $G_i = \frac{1}{R_i}$


KCL at e_1

$$(e_1 - V_0)G_1 + (e_1 - e_2)G_3 + (e_1)G_2 = 0 \quad (1)$$

KCL at e_2

$$(e_2 - e_1)G_3 + (e_2 - V_0)G_4 + e_2 G_5 - I_1 = 0 \quad (2)$$

e_1 and e_2

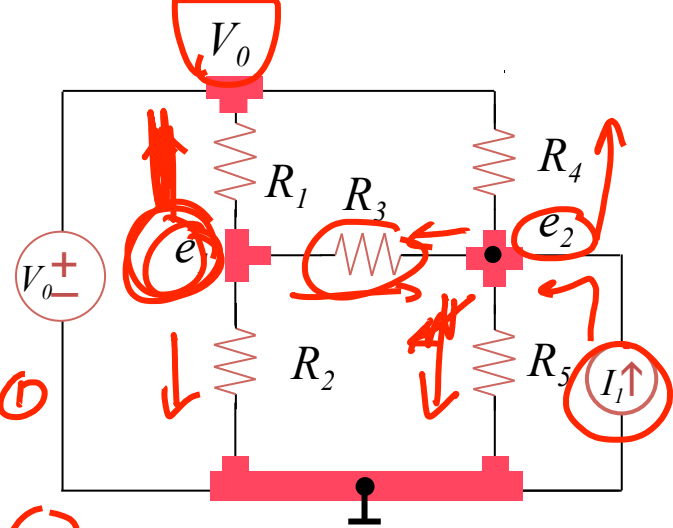

3. Write KCL for nodes, substituting device laws and KVL.

To avoid mistakes, use convention -
E.g., always sum the currents leaving a node

Step 4 of Node Method

KCL at e_1

$$(e_1 - V_0)G_1 + (e_1 - e_2)G_3 + (e_1)G_2 = 0 \quad \text{--- ①}$$


KCL at e_2

$$(e_2 - e_1)G_3 + (e_2 - V_0)G_4 + (e_2)G_5 - I_1 = 0 \quad \text{--- ②}$$

Move constant terms to RHS & collect unknowns

$$e_1(G_1 + G_3 + G_2) + e_2(-G_3) = V_0(G_1)$$
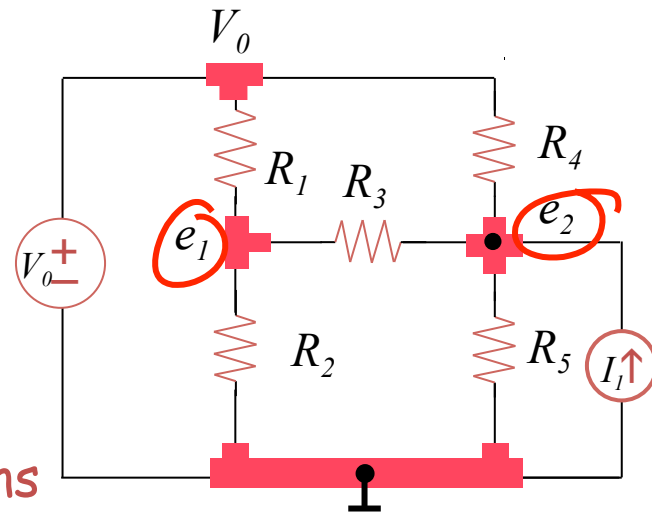
$$e_1(-G_3) + e_2(G_3 + G_4 + G_5) = V_0(G_4) + I_1$$



4. Solve for node voltages

2 equations, 2 unknowns \rightarrow Solve for e 's
(compare units)


Step 5 of Node Method

Once you have solved for e_1 and e_2 ,
easy to find branch v's and i's

For example:

$$v_1 = V_0 - e_1$$
$$i_1 = \frac{v_1}{R_1} = \frac{(V_0 - e_1)}{R_1}$$
$$\vdots$$

e 's

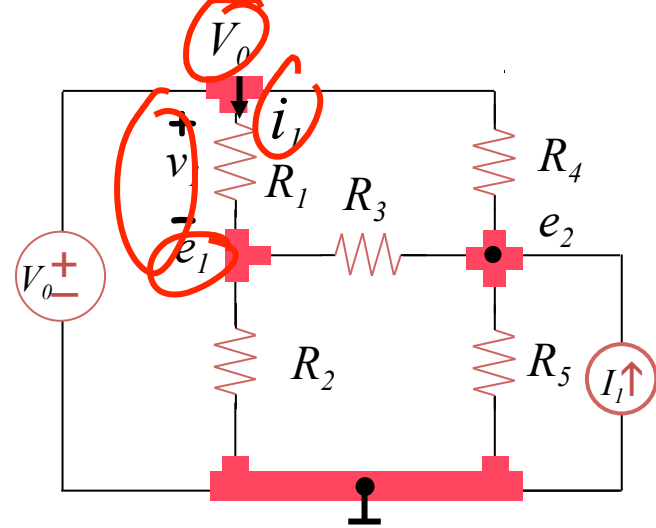

5. Back solve for
branch voltages and
currents

Revisit Step 4 of Node Method for Cultural Interest

$$e_1(G_1 + G_2 + G_3) + e_2(-G_3) = V_0(G_1) \quad - \textcircled{1} \quad 4. \text{ Solve for node voltages}$$

$$e_1(-G_3) + e_2(G_3 + G_4 + G_5) = V_0(G_4) + I_1 \quad - \textcircled{2}$$

In matrix form:

$$\begin{bmatrix} G_1 + G_2 + G_3 & -G_3 \\ -G_3 & G_3 + G_4 + G_5 \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \end{bmatrix} = \begin{bmatrix} G_1 V_0 \\ G_4 V_0 + I_1 \end{bmatrix}$$

conductivity matrix

unknown node voltages

sources

Step 4 of Node Method

4. Solve for node voltages

$$\left[\begin{array}{c|c} G_1 + G_2 + G_3 & -G_3 \\ \hline -G_3 & G_3 + G_4 + G_5 \end{array} \right] \begin{bmatrix} e_1 \\ e_2 \end{bmatrix} = \begin{bmatrix} G_1 V_0 \\ G_4 V_0 + I_1 \end{bmatrix}$$

$Ax = b$

Solve

$$\begin{bmatrix} e_1 \\ e_2 \end{bmatrix} = \frac{\left[\begin{array}{c|c} G_3 + G_4 + G_5 & G_3 \\ \hline G_3 & G_1 + G_2 + G_3 \end{array} \right] \begin{bmatrix} G_1 V_0 \\ G_4 V_0 + I_1 \end{bmatrix}}{(G_1 + G_2 + G_3)(G_3 + G_4 + G_5) - G_3^2}$$

$$e_1 = \frac{(G_3 + G_4 + G_5)(G_1 V_0) + (G_3)(G_4 V_0 + I_1)}{G_1 G_3 + G_1 G_4 + G_1 G_5 + G_2 G_3 + G_2 G_4 + G_2 G_5 + G_3^2 + G_3 G_4 + G_3 G_5}$$

$$e_2 = \frac{(G_3)(G_1 V_0) + (G_1 + G_2 + G_3)(G_4 V_0 + I_1)}{G_1 G_3 + G_1 G_4 + G_1 G_5 + G_2 G_3 + G_2 G_4 + G_2 G_5 + G_3^2 + G_3 G_4 + G_3 G_5}$$

(same denominator)

Notice: linear
in V_0, I_1 , no
negatives
in denominator
- we will use
this later

Step 4 of Node Method

E.g., solve for e_2 , given

$$\left. \begin{matrix} G_1 \\ G_5 \end{matrix} \right\} = \frac{1}{8.2K}$$

$$\left. \begin{matrix} G_2 \\ G_4 \end{matrix} \right\} = \frac{1}{3.9K}$$

$$G_3 = \frac{1}{1.5K}$$

$$I_1 = 0$$

$$e_2 = 0.6V_0$$

If $V_0 = 3V$, then $e_2 = 1.8V$
1.8 V

